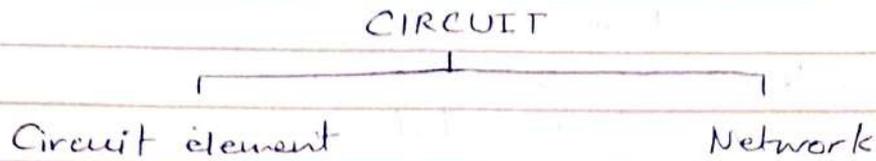



Electrical Engineering



Terminologies

- Network - connection of circuit elements
- Circuit element - parts of a circuit
- Branch - a wire connecting one side of circuit to another
- Junction - point of intersection of 2 or more wires
- Mesh / loop - a set of wires in a circuit which forms a complete path within the circuit. ~~like~~
- like a loop

<u>Branch</u>	<u>Loop</u>	<u>Circuit element</u>	<u>Network</u>
1. AB	1. ABDC	1. resistor	1. wires
2. CD	2. CDFE	2. capacitor	2. battery
3. EF	3. ABEF		

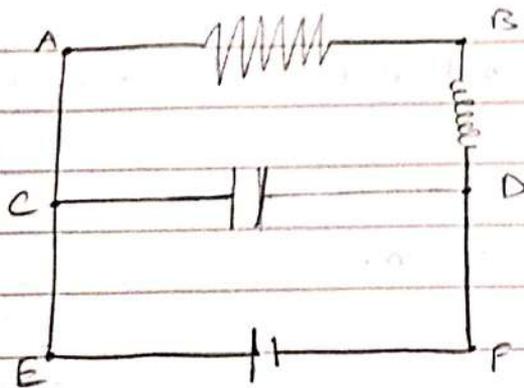

Electric Network

1. Active Vs. Passive
2. Linear Vs. Non-linear
3. Unilateral Vs. Bilateral
4. Lumped Vs. Distributed

1. Active Vs. Passive

- active - gives energy

- passive - receives energy

- active's examples include voltage and current source


- passive's examples include resistor, capacitance

2. Linear Vs. Non-linear

- linear

- no change in temp, volt and current.

- graph is a straight line

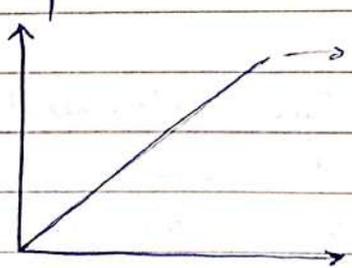-  temp, volt, current

- non-linear

- value of temp, volt are not constant.

- graph slope varies

3. Unilateral Vs. Bilateral

- Unilateral -

- one directional

→ diode (\rightarrow)

→ behaviour of circuit depends on direction of current

• bidirectional

→ behaviour / characteristics of circuit is independent of direction of current.

4. Lumped Vs. Distributed

• lumped.



→ network in which components are physically separable

→ transmission towers

• distributed

→ network in which components are not physically separable

→

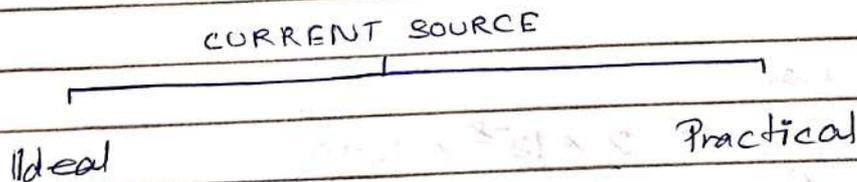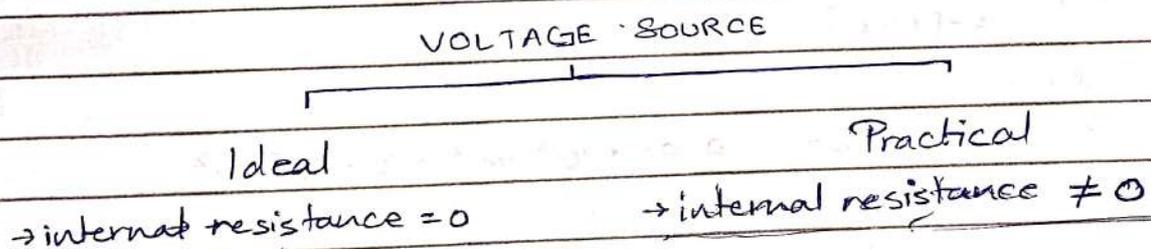

Resistance

Ability to oppose the flow of current.

• Factors that define resistance

→ length

- area ..
- temperature ..
- material ..

$$R \propto \frac{l}{A}$$

$$\Rightarrow R = \frac{\rho l}{A}$$

$$\rho = \text{res}$$

→ resistivity

→ unit: $\Omega \cdot m$

Q. A coil consists of 2000 turns of Cu wire having cross-sectional area 0.08 mm^2 . The mean length per turn is 80 cm and the resistivity of copper is $0.02 \cdot \mu \Omega \cdot m$. Find the resistance of coil and power absorbed by the coil when connected across 110 V of DC supply.

Ans.

Given

$$A = 0.08 \text{ mm}^2 = 0.08 \times 10^{-6} \text{ m}^2 = 8 \times 10^{-8} \text{ m}^2$$

$$l = 1600 \text{ m}$$

$$\rho = 2 \times 10^{-8} \Omega \cdot m$$

Solution

$$R = \frac{\rho l}{A} = \frac{2 \times 10^{-8} \times 1600}{8 \times 10^{-8}} = 400$$

$$P = V \times I$$

$$= \frac{V^2}{R}$$

[P = power
V = voltage
I = current]

Q. A resistance of conductor 1 mm^2 in cross section and 20 m long is 0.346Ω . Determine the specific resistance of the conducting material.

Ans. Given

$$l = 20 \text{ m}$$

$$R = 0.346 \Omega$$

$$A = 1 \times 10^{-6} \text{ m}^2$$

Solution

$$R = \frac{\rho l}{A}$$

$$0.346 = \frac{\rho (20)}{1 \times 10^{-6}}$$

$$\frac{0.346}{20 \times 10^{-6}} = \rho$$

$$\rho = \frac{346 \times 10^{-3}}{20}$$

$$\rho = 0.0173$$

Q. A resistance of conductor 1 mm^2 in cross section and 20 m long is 0.346Ω . Determine the specific resistance of the conducting material.

Ans. Given

$$A = 1 \times 10^{-6} \text{ m}^2$$

$$l = 20 \text{ m}$$

$$R = 0.346 \Omega$$

Solution

$$R = \frac{\rho l}{A}$$

Q.


Ohm's Law

$$V = IR$$

The circuit assuming physical conditions of conductor do not change,

$$I \propto V$$

Types of energy sources

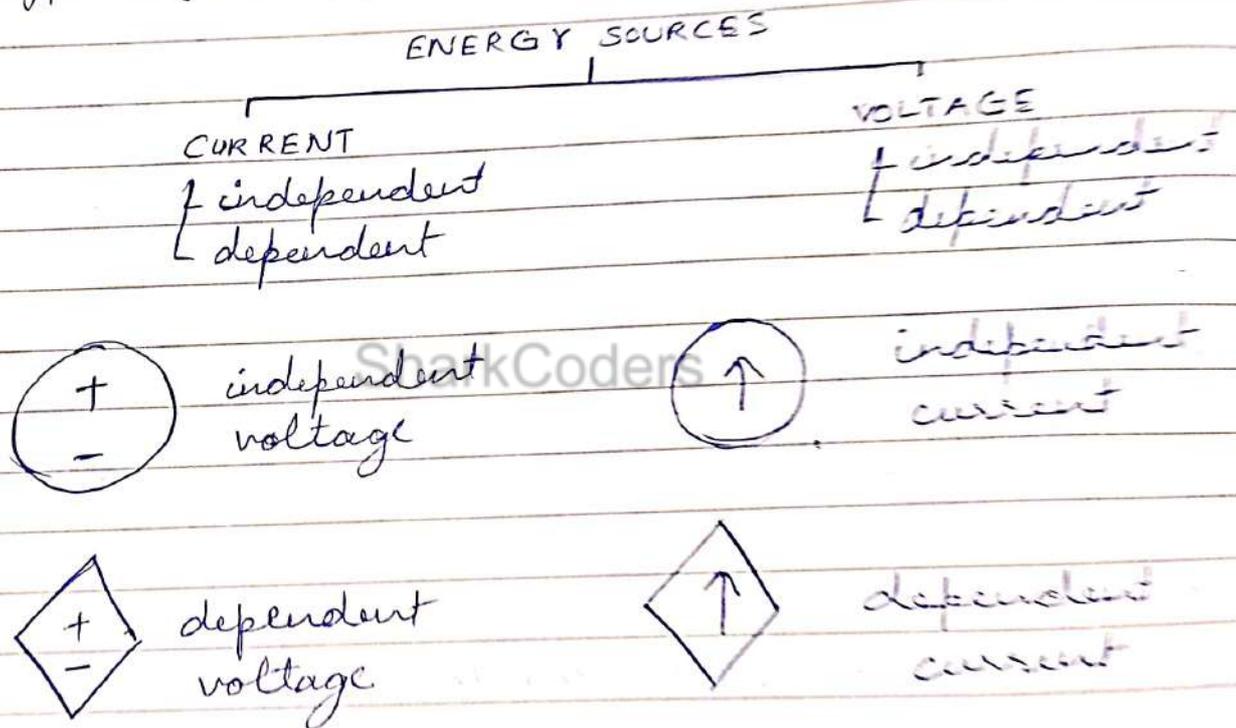

1. VCVS. (Voltage controlled voltage source)

$$\rightarrow k \cdot V_{oc}$$

2. CCVS

→ current controlled voltage source

$$\rightarrow k \cdot I_x$$


3. CCCS

→ current controlled current source

$$\rightarrow k \cdot I_x$$

4. VCCS

- voltage controlled current source
- $K \cdot V_x$

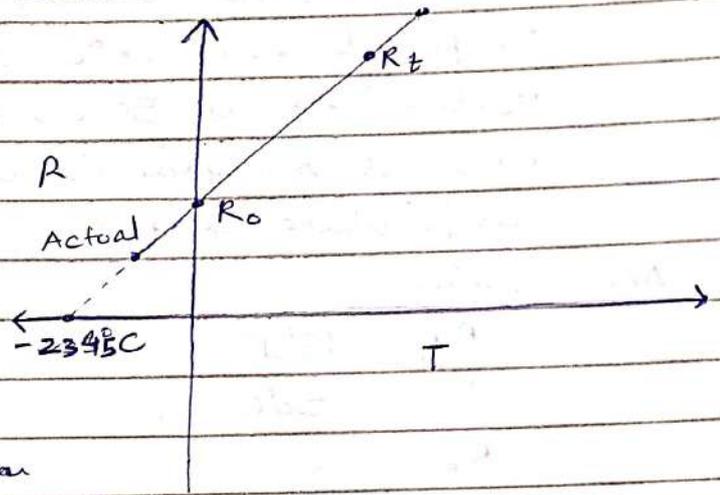~~Effect of~~ $R \propto T$ 

• the resistance of material

→ resistance of pure metal,

(Cu/Al) increases with temp

→ change in R is fairly regular for normal range

→ resistance of electrolyte insulator (mica, glass) and semic. (germanium, silicon) decreases with increase in temp.

→ R of alloy increases with temp. but is small and irregular.

→ theoretical value of Cu is 0° at $-2345^\circ C$

Temp. coefficient of R (RTC)

$$\bullet (R_t - R_0) \propto R_0$$

$$\Rightarrow (R_t - R_0) \propto T$$

Type of material

$$\bullet \alpha_0 = \frac{R_t - R_0}{R_0(t)} = \frac{\Delta R}{R_0(t)}$$

$$\bullet \Delta R = R_t - R_0$$

$$\bullet \frac{R_2}{R_1} = \frac{1 + \alpha_0 t_2}{1 + \alpha_0 t_1}$$

Q. The coil has a resistance of ~~30~~¹⁸ Ω when its mean temperature is 20°C and of 20Ω when its mean temperature is 50°C . Find its ~~mean~~^{mean} temperature in when its resistance is 21Ω and the surrounding temperature is 15°C .

Ans Given

$R_1 = 18\Omega$
 $T_1 = 20^\circ\text{C}$
 $R_2 = 20$
 $T_2 = 50^\circ\text{C}$

$R_t = R_0(1 + \alpha_0 t)$
 $R_1 = R_0(1 + \alpha_0 T_1)$

$R_t = \frac{1 + \alpha_0 t}{1 + \alpha_0 T_1}$

$\frac{21}{18} = \frac{1 + (0.004)t}{1 + (0.004)(20)}$

$\frac{7}{6} = \frac{1 + 0.004t}{1 + 0.08}$

Solution

$\frac{R_2}{R_1} = \frac{1 + \alpha_0 T_2}{1 + \alpha_0 T_1}$

$\frac{20}{18} = \frac{1 + \alpha_0(50)}{1 + \alpha_0(20)}$

$20 + 400\alpha_0 = 18 + 900\alpha_0$
 $2 = 500\alpha_0$

$\frac{2}{500} = \alpha_0$

$R = R_0(1 + t\alpha_0)$

$21 = R_0 \left(1 + \left(\frac{1}{250} \right) t \right)$

$\frac{R_t}{R_0} = \frac{1 + \alpha_0 t}{1 + \alpha_0}$

$20 + 400\alpha_0 = 18 + 900\alpha_0$
 $2 = 500\alpha_0$
 $\frac{1}{250} = \alpha_0$

$\frac{7}{6} = \frac{1 + 0.004t}{1.08}$

$\frac{1.08 \times 7 - 6}{6} = 0.004t$

$7.56 - 6$

$\frac{1.56}{6 \times 0.004} = t$

$\frac{280}{1560} \times \frac{390}{100} = 65 = t$
 $\frac{24}{126}$

Q. The resistance of the field coils of a dynamo is 173Ω at 16°C after ~~use~~. After working for 6 hours on full load, the resistance of the coil increases to 212Ω . Calculate:

- the temperature of the coils
- mean rise of temperature of the coil.

Assume that temperature coefficient of resistance is 0.00426°C at 0°C .

Ans.

Given

$$R_1 = 173 \Omega$$

$$T_1 = 16^\circ\text{C}$$

$$R_2 = 212 \Omega$$

$$T_2 = ?$$

$$\alpha_0 = 0.00426$$

Solution

$$R_T = R_0(1 + \alpha_0 T)$$

$$\frac{R_1}{R_2} = \frac{1 + (0.00426)(16)}{1 + (0.00426)T_2}$$

$$\frac{173}{212} = \frac{1.06816}{1 + 0.00426T_2}$$

$$212 = \frac{1.06816}{1 + 0.00426T_2} \times 173$$

$$1.23 = \frac{1.07}{1 + 0.00426T_2}$$

~~1.23~~

$$0.00426T_2 = \frac{1.07}{1.23} - \frac{1.23}{1.23} = -\frac{0.16}{1.23} = 0.00426$$

$$T_2 = \frac{+0.16}{1.23 \times 0.00426}$$

$$= \frac{0.16}{0.00518}$$

$$= 32$$

$$= 32$$

$$R = R_0(1 + \alpha_0 T)$$

$$R_2 = R_0(1 + \alpha_0 T_2)$$

$$\frac{R_2}{R_1} = \frac{1 + \alpha_0 T_2}{1 + \alpha_0 T_1}$$

$$R_50 = R_{20}(1 + \alpha_{50}(30))$$

$$954 = 900(1 + \alpha_{50}30)$$

$$1.06 = 1 + 30\alpha_{50}$$

$$\frac{0.06}{30} = \alpha_{50}$$

$$0.002 = \alpha_{50}$$

$$\frac{1.23}{1.23} - \frac{1.07}{1.23} = \frac{0.16}{1.23}$$

Given

$$R_1 = 173$$

$$T = 16^\circ\text{C}$$

$$R_2 = 212 \Omega$$

$$\alpha_0 = 0.00426.$$

Solution

$$R_2 = R_0(1 + \alpha_0 T_2)$$

$$R_1 = R_0(1 + \alpha_0 T_1)$$

$$173 = R_0(1 + 0.00426 \times T_2)$$

$$212 = R_0(1 + 0.00426 \times 16)$$

$$0.82 = 1 + 0.00426 T_2$$

$$+0.6 \quad 1.07$$

SharkCoders

$$0.82 \times 1.07 - 1 = T_2$$

$$0.00426$$

$$0.88 - 1$$

$$0.00426$$

$$0.12$$

$$0.00426$$

- Q. Two coils connected in series have resistances of $600\ \Omega$ and $300\ \Omega$ and temperature coefficient of 0.1% and 0.4% for $^{\circ}\text{C}$ at 20°C respectively. Find the resistance of combination at temperature of 50°C . What is the effective temperature coefficient of the combination at 50°C .

Ans.

Given

$$R_1 = 600\ \Omega$$

$$R_2 = 300\ \Omega$$

$$R_{20} = 300\ \Omega$$

$$\alpha_1 = 0.001$$

$$\alpha_2 = 0.004$$

$$T_1 = 20^{\circ}$$

$$\begin{aligned} R_1 &= 600(1 + \alpha(30)) \\ &= 600(1 + 0.001 \times 30) \\ &= 600(1.03) \\ &= 618 \end{aligned}$$

$$\begin{aligned} R_2 &= 300(1 + 0.004(30)) \\ &= 300(1.12) \\ &= 336 \end{aligned}$$

Solution

SharkCoeders

$$R_1 = R_0(1 + \alpha T_1)$$

$$R_2 =$$

$$R = 954\ \Omega$$

$$R_1 = 600(1 + \alpha_0 T_{50})$$

$$R_1 = 600(1 + 0.001 \times 50)$$

$$R_1 = 600 \times (1.05)$$

$$= 6 \times 105$$

$$= 630\ \Omega$$

$$R_2 = 300(1 + 0.004 \times 50)$$

$$= 300(1.2)$$

$$= 360$$

Q. A carbon resistor has a resistance of $800\ \Omega$ at 20°C . Determine its resistance at

a) $+100^\circ\text{C}$

b) -100°C

The temperature coefficient of resistance of C at 20°C is $-0.00047/^\circ\text{C}$.

Ans. Given

$$R_0 = 800\ \Omega$$

$$T_0 = 20^\circ\text{C}$$

$$\alpha_0 = -0.00047$$

a) $R = R_0(1 + (-0.00047)(100 - 20))$

$$R = 800(1 - 0.00047 \times 80)$$

$$R_{100} = 769.92$$

SharkCoders

b) $R = 800(1 + (-0.00047)(-100 - 20))$


$$= 800(1 + (-0.00047)(-120))$$

$$= 800(1 + 0.0564)$$

$$= 845.12$$

Series parallel connections of Resistor Resistances

1. Series connection

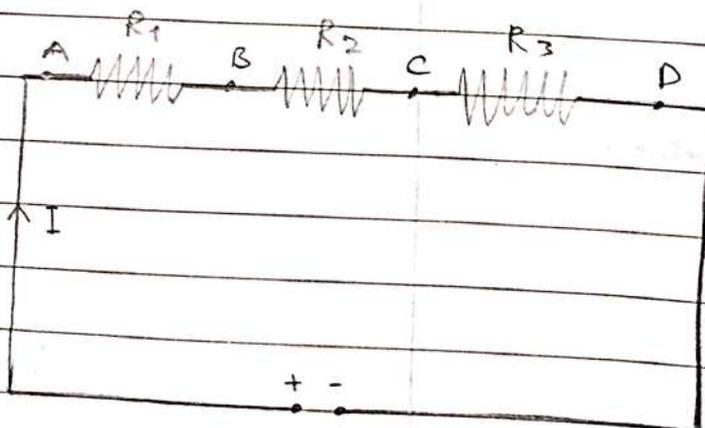

$$V = V_1 + V_2 + V_3 + \dots$$

By Ohm's Law,

$$IR = IR_1 + IR_2 + IR_3 + \dots \quad \text{--- ①}$$

$$\therefore R = R_1 + R_2 + R_3 + \dots \quad \text{--- ②}$$


$$\therefore \frac{1}{G} = \frac{1}{G_1} + \frac{1}{G_2} + \frac{1}{G_3} \quad [G = \text{conductance}]$$

• resistors are arranged along one wire.

• current is constant

Voltage division rules (series)

• determining V across each resistance

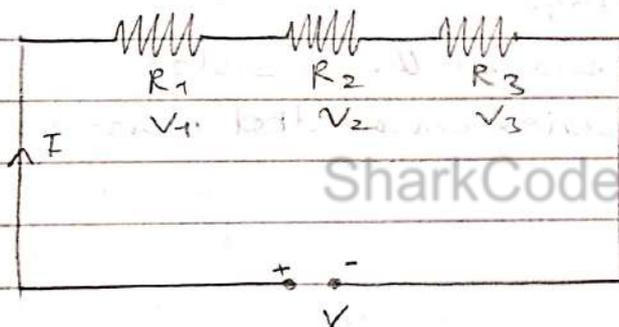

$$\cdot V = I(R_1 + R_2 + R_3) \quad \text{[From ①]}$$

$$\Rightarrow V = IR \quad \text{[From ②]}$$

$$\Rightarrow I = \frac{V}{R_1 + R_2 + R_3}$$

$$\cdot V_1 = IR_1$$

$$V_2 = IR_2$$

$$V_3 = IR_3$$

$$\cdot V_1 = V \cdot \frac{R_1}{R}$$

$$V_2 = V \cdot \frac{R_2}{R} \quad \text{and} \quad V_3 = V \cdot \frac{R_3}{R}$$

Practical application of VDR

• when resistances are connected in series across voltage source.

• the volt drop across resistor can be calculated easily

• the current I flowing through all the series connector is same.

~~• V across resistor in series circuit = total voltage~~
* voltage


• V_1 = volt across resistor in series circuit

V_0 = total voltage

R_1 = resistance across the resistor

R = sum of all series connected resistances

Parallel connection

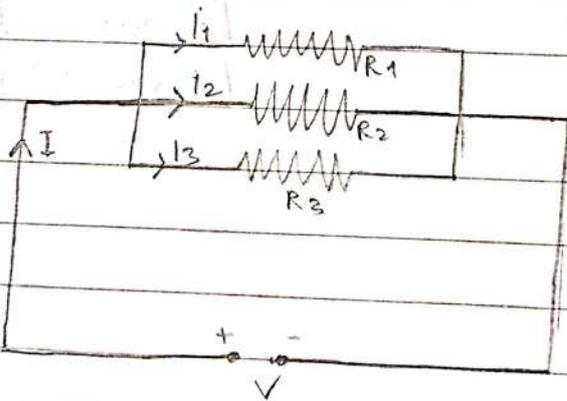

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

$$\Rightarrow G = G_1 + G_2 + G_3 + \dots$$

$$I = I_1 + I_2 + I_3$$

By ohm's law,

$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$


Current division rule (parallel)

• ~~used~~ useful for finding the current when resistances are connected in a parallel arrangement.

• the voltage applied across the || circuit is same, V

• the current supplied by the source is I .

• the current flowing through || resistances is I_1 and I_2 .

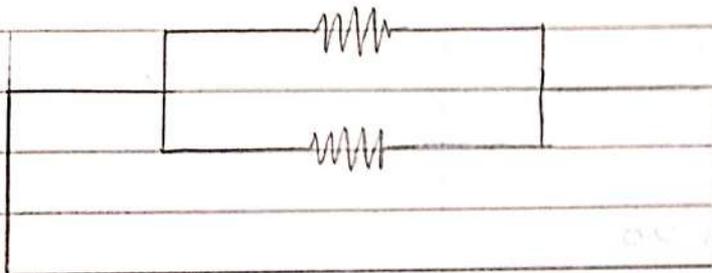

SharkCoders

$$I = I_1 + I_2 + \dots$$

By ohm's law,

$$I_1 = \frac{V}{R_1} \quad \text{and} \quad I_2 = \frac{V}{R_2}$$

$$\Rightarrow V = I_1 R_1 = I_2 R_2$$

$$\Rightarrow I_2 = \frac{I_1 R_1}{R_2} \quad \text{--- (1)}$$

$$I = I_1 + I_2$$

$$I = I_1 + \frac{I_1 R_1}{R_2}$$

$$I = \left(1 + \frac{R_1}{R_2}\right) I_1$$

$$\therefore I_1 = \left[\frac{R_2}{(R_1 + R_2)} \right] I$$

$$I_2 = \left[\frac{R_1}{(R_1 + R_2)} \right] I$$

- current flowing through resistor in || circuit = I
- source current = I
- value of opposite resistance = R_2/R_1
- sum of all parallelly connected resistors = R

Q. 3 resistors of 8.4Ω , 6.8Ω , and 4.8Ω are connected in series across 100V supply. Find :
a) total R_e
b) current
c) voltage across each resistor


Ans. Given
 $R_1 = 8.4$
 $R_2 = 6.8$
 $R_3 = 4.8$
 $R = 20$
 $V = 100$

a) $R = R_1 + R_2 + R_3 = 20$

b) $V = IR$
 $100 = I \times 20$
 $I = 5 A$

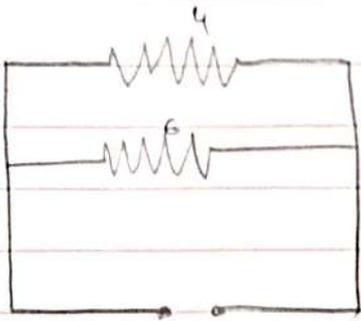c) $V_1 = 5 \times 8.4 = 42.0 V$
 $V_2 = 5 \times 6.8 = 34.0 V$
 $V_3 = 5 \times 4.8 = 24.0 V$

Q. two resistors (4Ω and 6Ω) are connected parallel if the current supplied by a source is Find the R_e and current through each branch
Ans. (NEXT PAGE)



$R_1 = 4 \Omega$
 $R_2 = 6 \Omega$
 $I = 30 A$
 R_{eq}

a) $\frac{1}{R_{eq}} = \frac{1}{4} + \frac{1}{6} = \frac{10}{24} = \frac{5}{12}$

$\Rightarrow R_{eq} = 2.4$

b) $V = I R_{eq}$
 $V = 1 R$
 $V = 2.4 \times 30$
 $V = 72$

$V = I_1 R_1$
 $72 = I_1 (4)$
 $18 = I_1$


$I_2 = \frac{V}{R_2} = \frac{72}{6} = 12$

$\therefore I_1 = 18 A$
 $I_2 = 12 A$

$I_1 = \left(\frac{R_2}{R_1 + R_2} \right) \cdot I$
 $= \frac{6 \times 30}{10}$
 $= 18 A$


$I_2 = \left(\frac{R_1}{R_1 + R_2} \right) \cdot I$
 $= \frac{4 \times 30}{10}$
 $= 12 A$

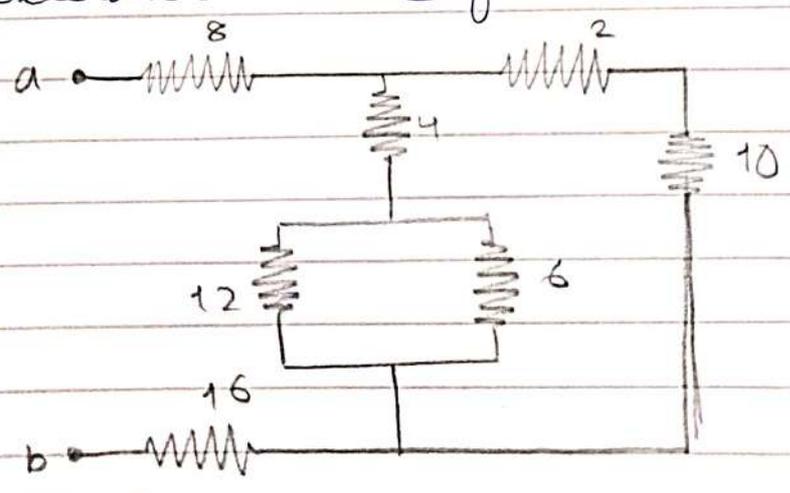Q. Determine the R_{eq} for the circuit shown.




$$R_{eq1} = \frac{18}{72} = \frac{9}{36} = \frac{1}{4}$$

$$R_m = 4$$

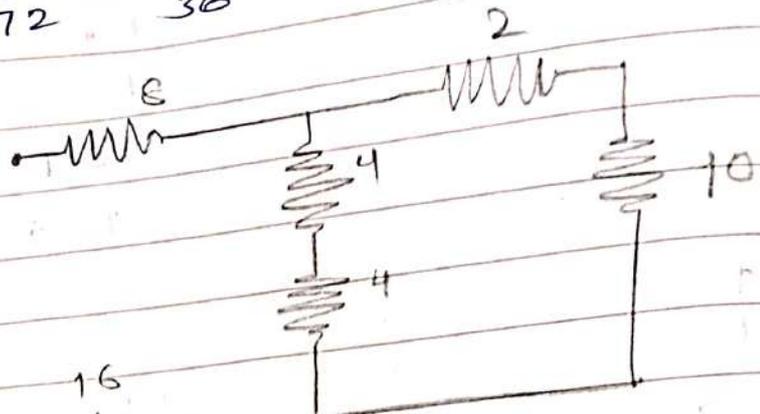

$$R_m = 4 + 4 = 8$$

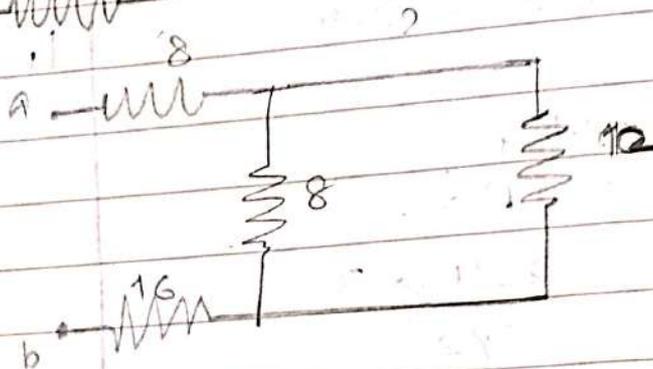


$$\frac{8 \times 20}{8 + 20} = \frac{160}{28} = \frac{40}{7}$$

$$\frac{20}{96} = \frac{5}{24}$$



$$R_3 = \frac{24}{5} = 4.8$$


$$\therefore R_e = 28.8$$

SharkCoders

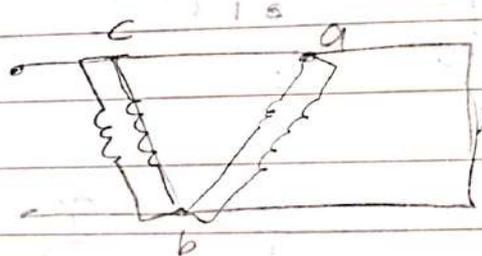

Q. Find the R_e for the circuit shown.

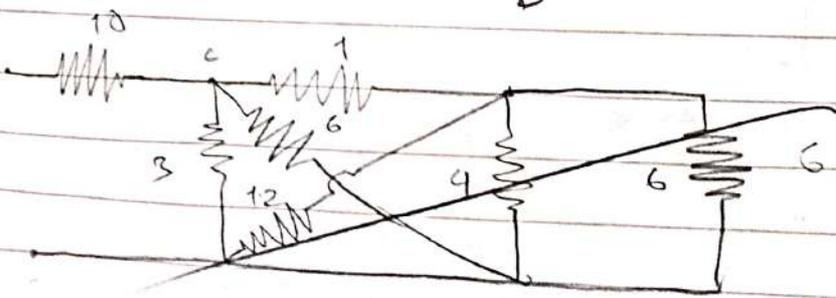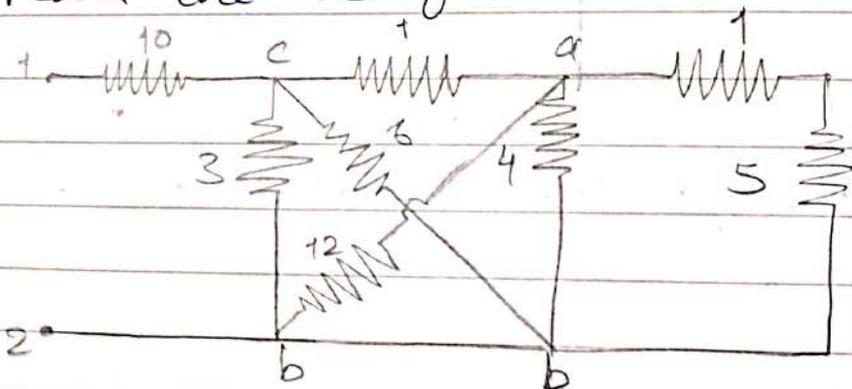

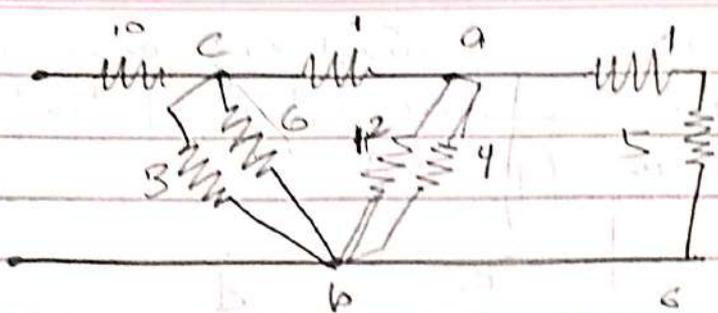


$$\frac{10 \cdot 4}{40} = \frac{10}{4}$$

$$\frac{10}{4} \cdot \frac{1}{12} = \frac{10}{48}$$

$$\frac{10}{48} \cdot \frac{1}{3} = \frac{10}{144}$$

$$\frac{10}{144} \cdot \frac{1}{5} = \frac{10}{720}$$
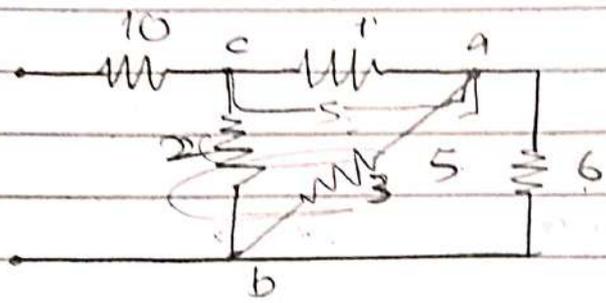
$$\frac{10}{720} \cdot \frac{1}{6} = \frac{10}{4320}$$




$$\frac{5}{5} = 1.2$$


$$\frac{6}{5} = 1.2$$




Q Find R_{12} in the following figure.

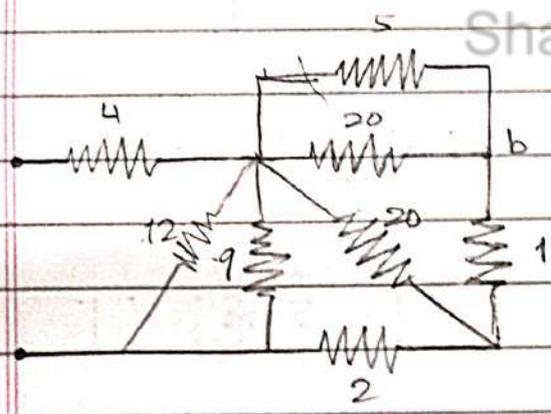

SharkCoders

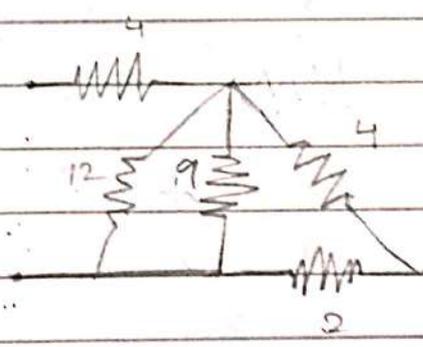


$R_{12} = 6.77$

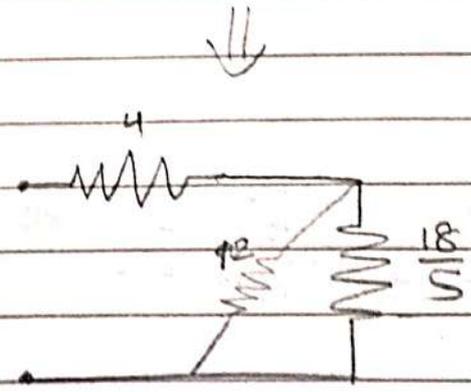


$R_{eq} = 15.75$



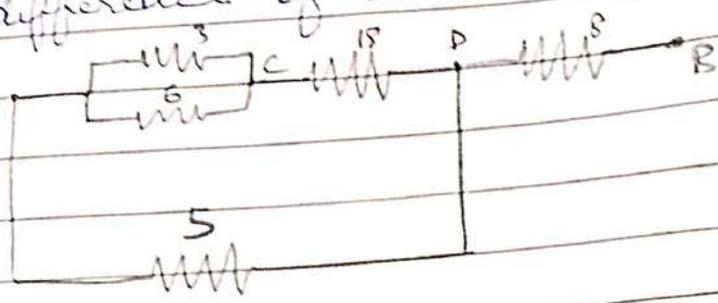
Q.1. Calculate R_e of this combination and the voltage across each resistor when potential difference of 60V is applied.



Q.2. Find R_e of the following.





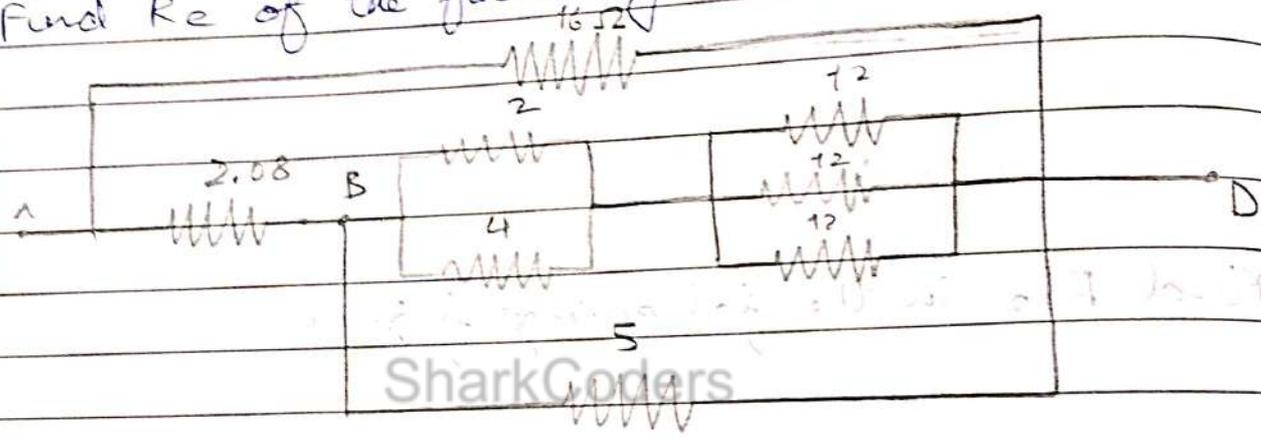


Q.1.

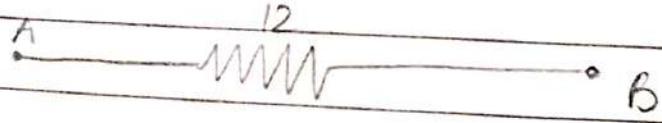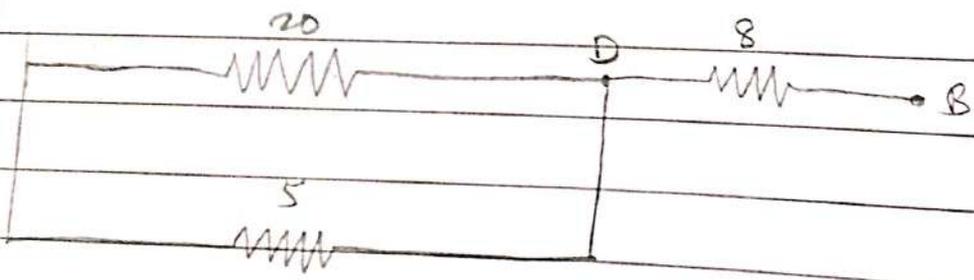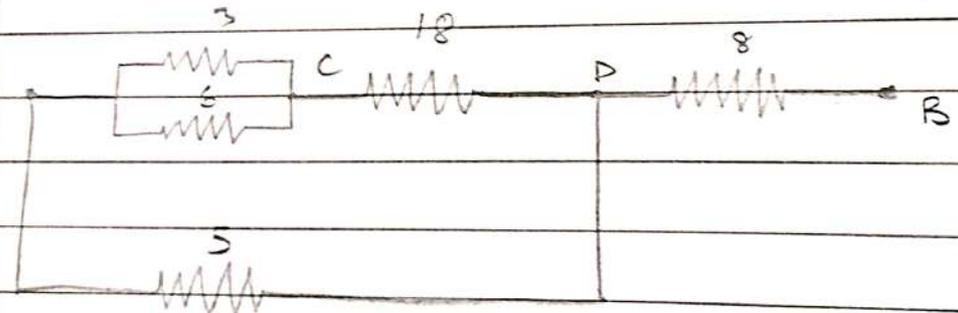





$R_{eq} = 12 \Omega$

Q2.

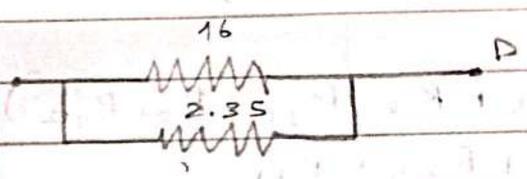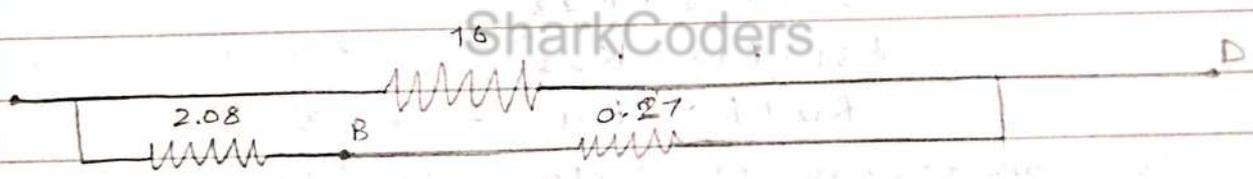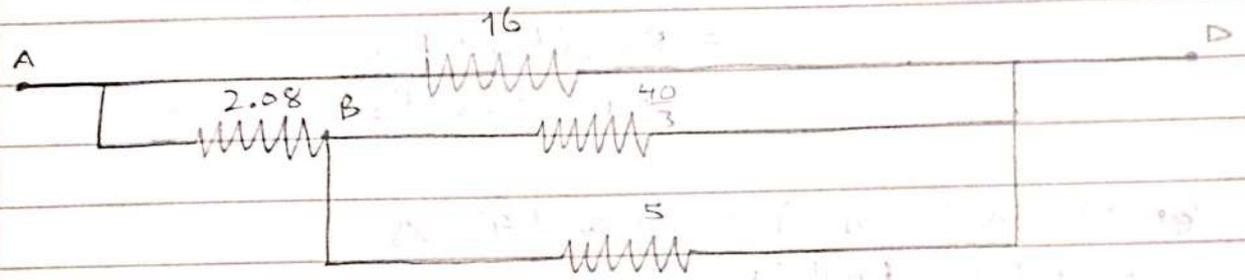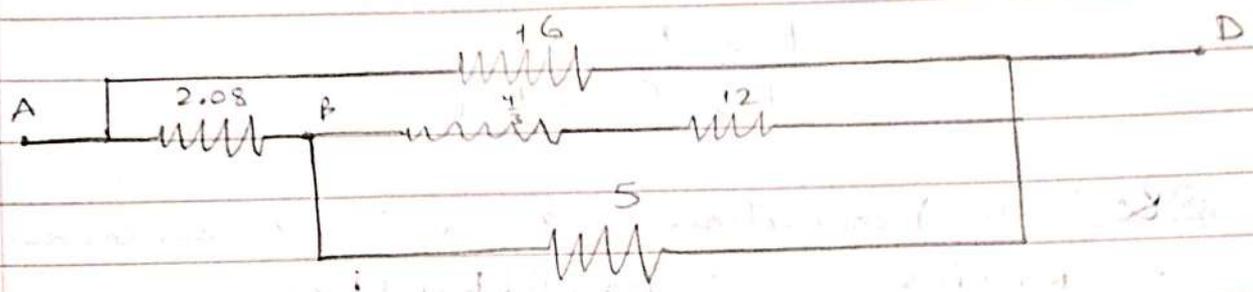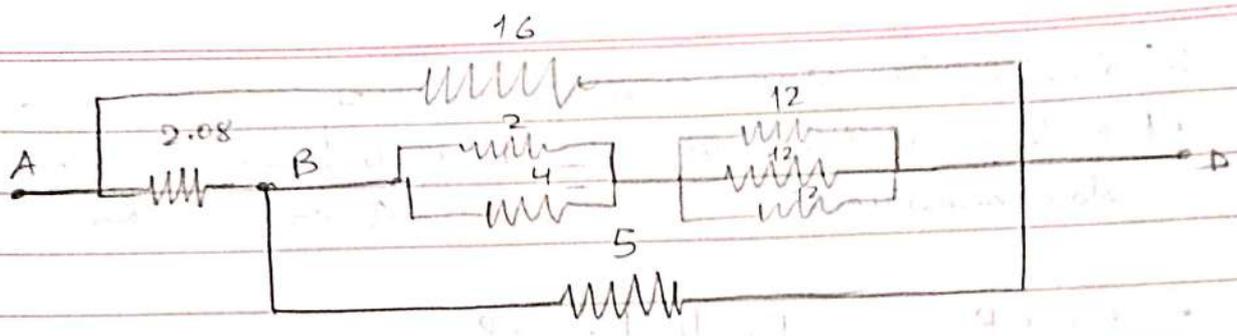

$R_{eq} = 0.49 \Omega$

Star-delta transformation

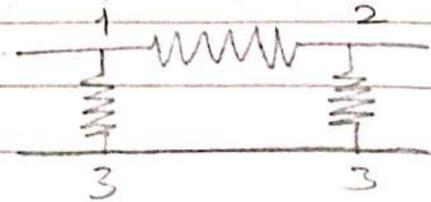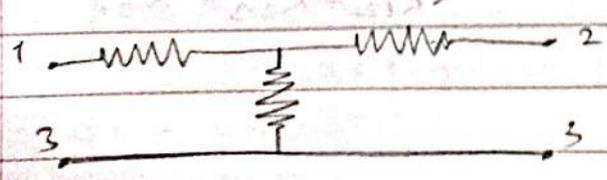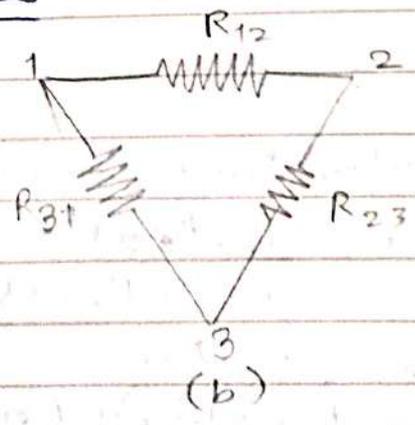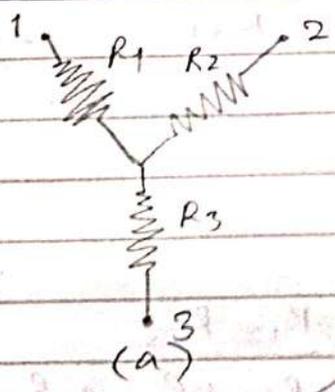

ation
of terminals ① ② ③ in
Δ connection.

$$\begin{aligned} \bullet R_1 + R_2 &= R_{12} \parallel (R_{23} + R_{31}) \\ &= \frac{R_{12} (R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}} \end{aligned} \quad \text{--- ①}$$

② & ③ in Y connection = ② and ③ in Δ connection.

$$\begin{aligned} \bullet R_2 + R_3 &= R_{23} \parallel (R_{31} + R_{12}) \\ &= \frac{R_{23} (R_{31} + R_{12})}{R_{12} + R_{23} + R_{31}} \end{aligned} \quad \text{--- ②}$$

③ and ① in Y = ③ and ① in Δ

$$\begin{aligned} R_3 + R_1 &= R_{31} \parallel (R_{12} + R_{23}) \\ &= \frac{R_{31} (R_{12} + R_{23})}{R_{12} + R_{23} + R_{31}} \end{aligned} \quad \text{--- ③}$$

$= R_{12} R_{31} + R_{23} R_{31}$

For conversion of delta into star,
Adding ①, ②, and ③,

$$2(R_1 + R_2 + R_3) = \frac{2(R_{12}R_{23} + R_{23}R_{31} + R_{31}R_{12})}{R_{12} + R_{23} + R_{31}}$$

$$\therefore R_1 + R_2 + R_3 = \frac{R_{12}R_{23} + R_{23}R_{31} + R_{31}R_{12}}{R_{12} + R_{23} + R_{31}} \quad \text{--- ④}$$


Subtracting ② from ④,

$$R_1 = \frac{R_{12}R_{31}}{R_{12} + R_{23} + R_{31}}$$

~~$$R_2 = \frac{R_{23}R_{31}}{R_{12} + R_{23} + R_{31}}$$~~

$$R_2 = \frac{R_{12}R_{23}}{R_{12} + R_{23} + R_{31}}$$

$\Delta \rightarrow *$ transformation

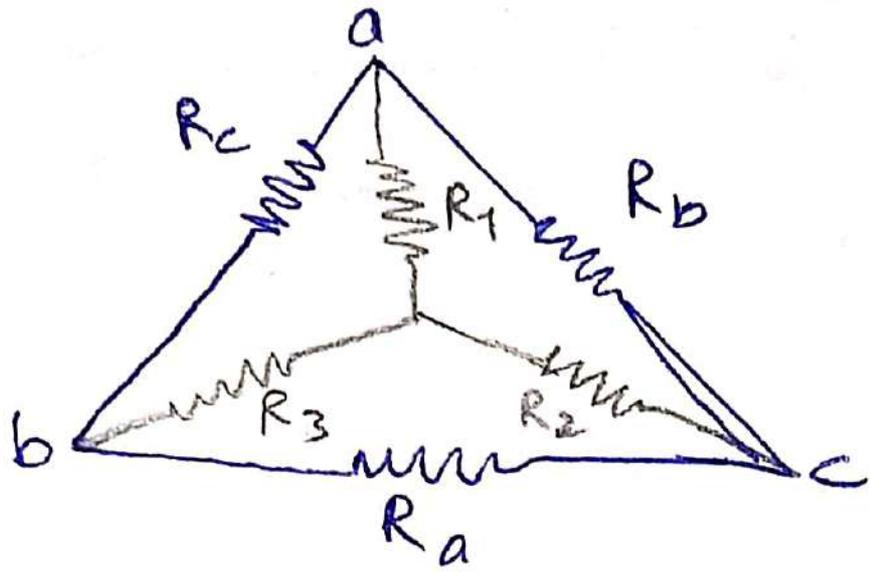


$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$* \rightarrow \Delta$ transformation

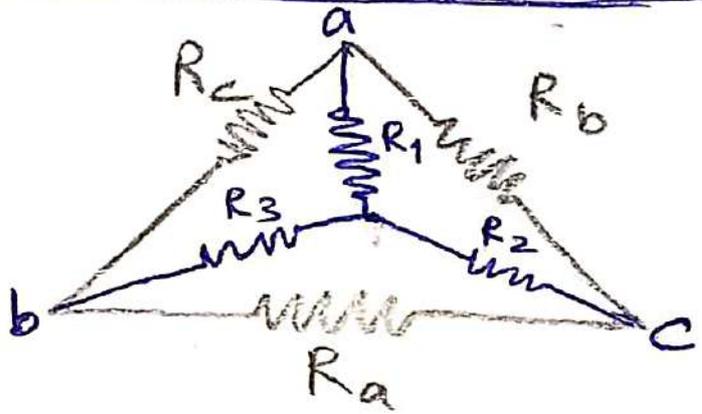

$$R_a = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$

$$R_b = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_c = R_1 + R_3 + \frac{R_1 R_3}{R_2}$$

$$R_3 = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{31}}$$

$$R_3 = \frac{R_{23} R_{31}}{R_{12} + R_{23} + R_{31}}$$

④, ⑤, ⑥ are the formulae for converting Δ -connection to star connection.

It is seen that the R of any branch of the equivalent star connection is obtained by multiplying the adjacent resistances of the branch and dividing by the sum of the 3 resistances.

2. Star - delta transformation

$$R_{12} = \frac{R_1 (R_{12} + R_{23} + R_{31})}{R_{31}}$$

$$R_{23} = \frac{R_2 (R_{12} + R_{23} + R_{31})}{R_{12}}$$

$$R_{31} = \frac{R_3 (R_{12} + R_{23} + R_{31})}{R_{23}}$$

Multiply ⑥ and ⑦, ④ ⑤ and ⑥, and ⑦ × ⑤

~~R₁₂~~

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_{12}^2 R_{23} R_{31} + R_{23}^3 R_{31} R_{12} + R_{31}^2 R_{12} R_{23}}{(R_{12} + R_{23} + R_{31})^2}$$

$$= \frac{R_{12} R_{23} R_{31} (R_{12} + R_{23} + R_{31})}{(R_{12} + R_{23} + R_{31})^2}$$

$$= \frac{R_{12} R_{23} R_{31}}{R_{12} + R_{23} + R_{31}}$$


Divide (8) / (7)

$$\frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = \frac{R_{12} R_{23} R_{31}}{R}$$

SharkCoders

Join our whatsapp group

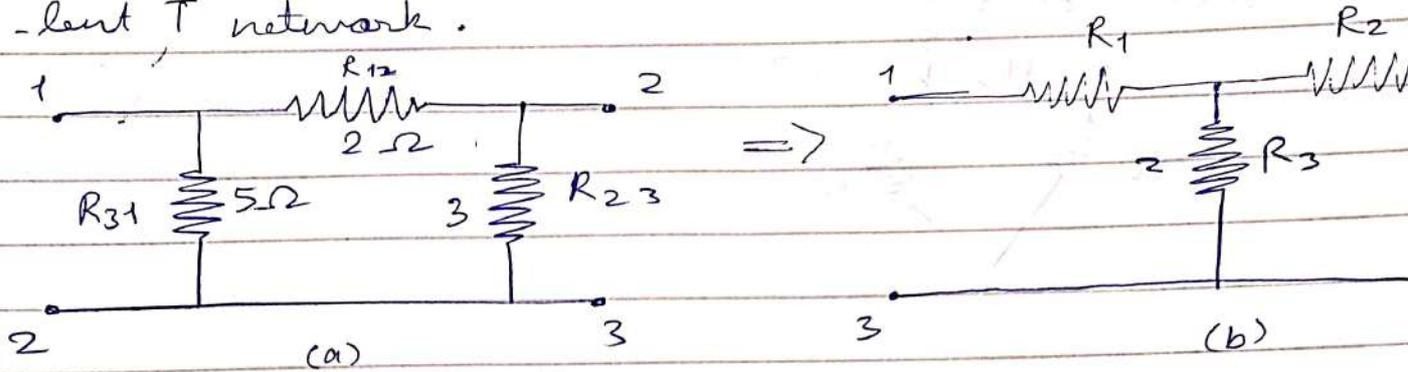Q. Convert the π network in figure A to its equivalent T network.



Ans.

Given

$$R_{12} = 2\Omega$$

$$R_{23} = 3\Omega$$

$$R_{31} = 5\Omega$$

Total To find

$$R_1$$

$$R_2$$

$$R_3$$

Solution

$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$R_1 = \frac{2 \times 5}{10} = 1$$

$$R_2 = \frac{R_{23} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$= \frac{3 \times 2}{10} = \frac{3}{5} = 0.6$$


$$R_3 = \frac{R_{23} R_{31}}{R_{12} + R_{23} + R_{31}} = \frac{3 \times 5}{10} = \frac{3}{2} = 1.5$$

$$\therefore R_1 = 1$$

$$R_2 = 0.6$$

$$R_3 = 1.5$$

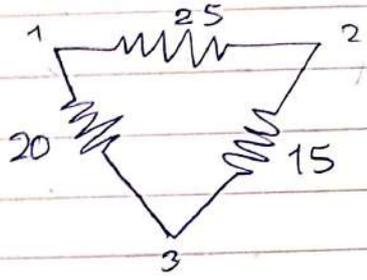Q. Convert the Δ network in figure into its equivalent star network



<u>Given</u>	<u>To find</u>
$R_{12} = 25$	R_1
$R_{23} = 15$	R_2
$R_{31} = 20$	R_3


Solⁿ

$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}} = \frac{25 \times 20}{25 + 15 + 20} = \frac{500}{60} = 8.34$$

$$R_2 = \frac{R_{23} R_{12}}{R_{12} + R_{23} + R_{31}} = \frac{15 \times 25}{60} = 6.25$$

$$R_3 = \frac{R_{31} R_{23}}{R_{12} + R_{23} + R_{31}} = \frac{20 \times 15}{60} = 5$$

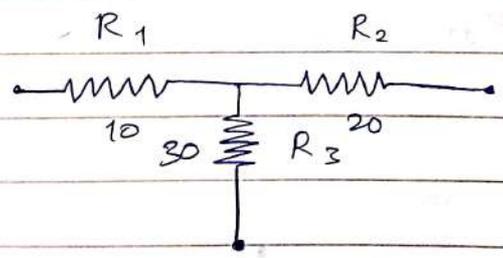Q. Transform the T-network into delta network.



<u>Given</u>	<u>To find</u>
$R_1 = 10 \Omega$	R_{12}
$R_2 = 20 \Omega$	R_{23}
$R_3 = 30 \Omega$	R_{31}

$$R_{12} = \frac{R_1 (R_{12} + R_{23} + R_{31})}{R_{13}}$$

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_{12} = 10 + 20 + \frac{200}{30}$$

$$= 30 + 6.67 = 36.67$$

$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$

$$= 20 + 30 + \frac{600}{10}$$

$$= 110$$

$$R_{31} = R_3 + R_1 + \frac{R_3 R_1}{R_2}$$

$$= 30 + 10 + \frac{300}{20}$$


$$= 40 + 15 = 55$$

$$\therefore R_{12} = 36.67$$

$$R_{23} = 110$$

$$R_{31} = 55.$$

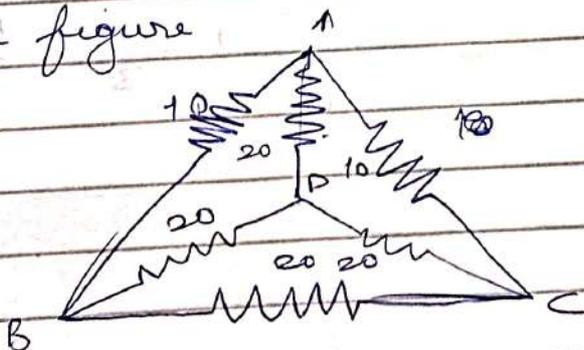a. Find the R between point A and point D in the given figure



$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}} = \frac{10 \times 20}{10 + 20 + 20} = \frac{200}{50} = 4 \Omega$$

$$= \frac{20 \times 20}{20 + 3} = \frac{400}{60} = 6.67 \Omega$$

So 10Ω and $20/3$ are connected in series.



$$10 + \frac{20}{3} = \frac{50}{3} \Omega$$

10 and $20/3$ are connected in series.

$$10 + \frac{20}{3} = \frac{50}{3} \Omega$$


So $50/3$ and $50/3$ are connected in parallel,
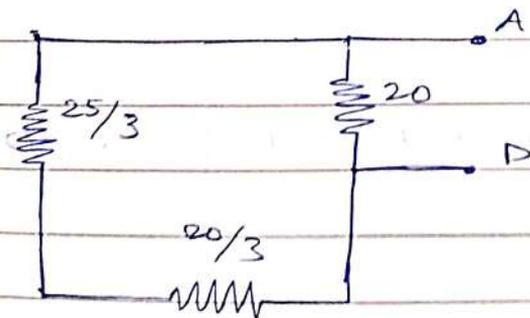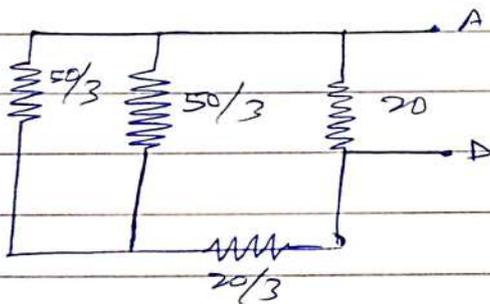
$$\frac{\frac{50}{3} \times \frac{50}{3}}{\frac{50}{3} + \frac{50}{3}} = \frac{(2500) \left(\frac{3}{100}\right)}{\frac{100}{3}} = \frac{25}{3} \Omega$$



$\frac{25}{3}$ and $\frac{20}{3}$ are in series

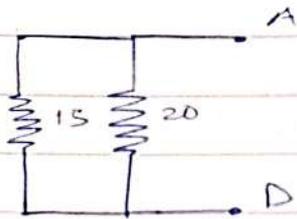
$$\frac{25}{3} + \frac{20}{3} = \frac{45}{3} = 15 \Omega$$




15Ω and 20Ω are connected in parallel.

$$R(AD) = \frac{15 \times 20}{15 + 20} = \frac{60}{7} = 8.57 \Omega$$

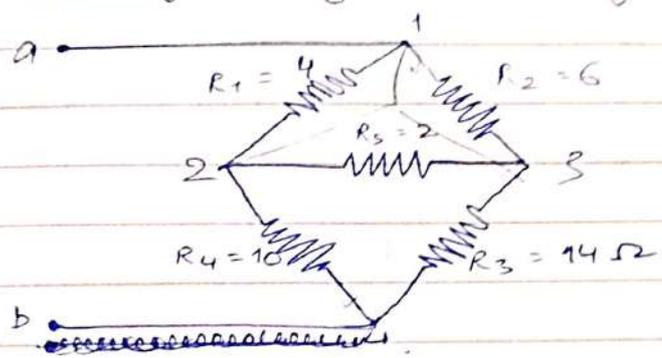Q. Find the R of the bridge circuit in the following figure by using Δ transformation method.



SharkCoders

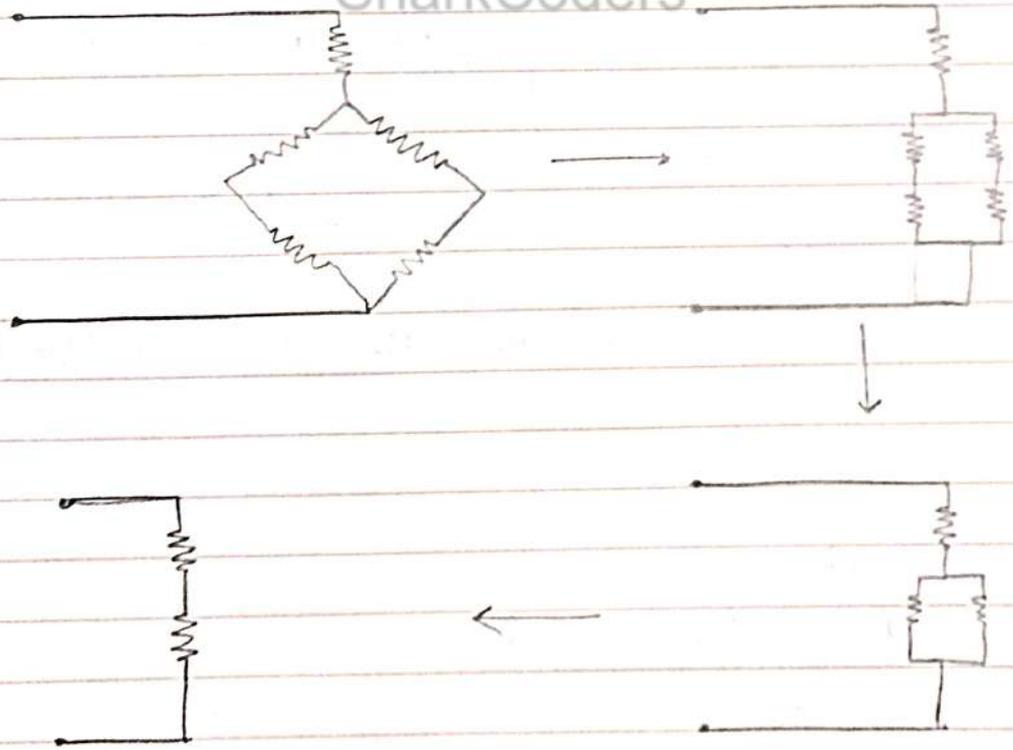

- lab record

Lab

• lab records and observation notebook.

• lab records

→ exp. no.

→ exp. date.

→ obj.

→ apparatus required

→

S.No.	Name of equipment	Quantity	Range	Type (DC/AC)

→ Theory + formula + circuit

→ Procedure

• ~~work~~

→ one side plane and one side lined

→ circuit diagram for plane side

→ obs. table on plane side

→ obs. table

→ calculation (on plane side)

→ result

→ Conclusion (error < 10%)

→ precautions

→ questions

• observation notebook.

→ lock up ~~the~~ lab r.

Lists of experiments

1. To study measuring instruments and safety precautions while working on electrical systems
2. To study and verify Kirchoff's Current Law (KCL) and Kirchoff's Voltage Law (KVL)
3. To study the V-I characters of an incand-
-escent lamp.
4. To perform an open circuit test on a single
- phase transformer
5. To perform a short circuit test on a single
- phase transformer
6. To perform an open circuit test on a single
- phase transformer
7. To measure 3-phase power by using 2
Wattmeter methods
8. To study and verify Thevenin's and Norton's
- theorem
9. To study and verify the superposition theorem
10. To study the R-L-C series and parallel
circuits.
11. To study Star & Delta connection in a

classmate

Date _____

Page _____

3-phase AC circuit.

11. To perform measurement of resistance of armature winding, series field winding and shunt field winding of a DC machine.

12. To


KCL

The 1st law states that the algebraic sum of the current meeting at a point or junction is zero. OR

The incoming current = outgoing current.
Consider a case of few conductors meeting at a point

A as shown in figure. Some conductors have current leading to point A where as some have a current leading away from point A assuming that incoming current to be i_1, i_2, i_3, i_4 and outgoing i_5 .

we have.

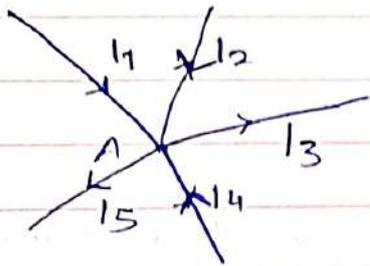

$$i_1 + i_2 + i_3 + i_4 - i_5 = 0$$

$$i_1 + i_2 + i_3 + i_4 = i_5$$

incoming currents = outgoing currents.


SharkCoders

The algebraic and resistances in each of the conductors in a closed path in a network + the algebraic sum of the e.m.f. in that path.

Kirchoff's Voltage Law

$$\sum I \cdot R + \sum E = 0$$

(closed path)

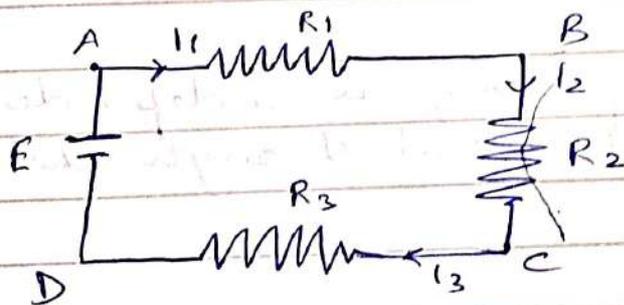

$$I_1 R_1 + I_2 R_2 + I_3 R_3 = E$$


Determination of Kirchhoff's Law

In applying, Kirchhoff's law to specific problems particular attention should be given to the algebraic sign of V law and emf following sign convention are suggested.

1. sign of battery emf.




(Rise in voltage)

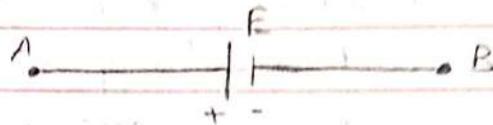

(Fall in voltage)


- rise in voltage should be +ve
- fall in voltage should be -ve.
- it is clear that we go from -ve terminal of battery to its +ve terminal as shown in figure A.
- there is rise in potential hence this voltage should be given +ve sign if on other hand, we go from +ve terminal to -ve terminal, then there is fall in potential. voltage should be received by -ve side.
- the sign of battery e.m.f. is independent of the direction of current ~~to that~~ through that branch.

2. sign of IR drop.

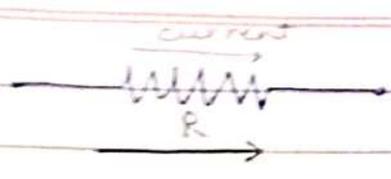

(fall in volt)

$$V = -IR$$

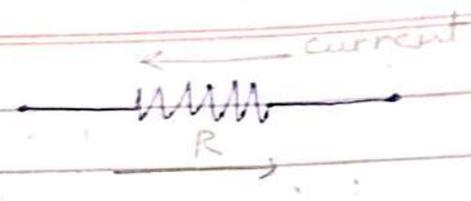

(rise in volt)


$$V = IR$$

Now, consider the case of R: if we go through the resistance in the same direction as the current then there is a fall in potential because current flows from higher to lower potential. Therefore, this voltage fall should be taken -ve.

However, if you go in the direction against the current, then there is a rise of voltage. This voltage rise is given a +ve sign.

SharkCoders

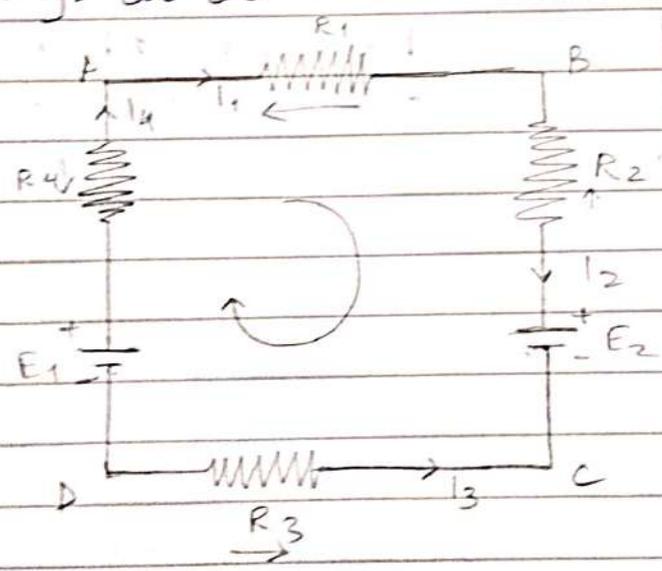it is clear that the sign of voltage drop across resistance depends on the direction of current through that resistance but it is independent of any other source the polarity of any other source of em.f. in the circuit under consideration.




- $I_1 R_1 = +ve$ (fall) ^{rise}
- $I_2 R_2 = +ve$ (fall) ^{rise}
- $E_2 = -ve$ (fall)
- $I_3 R_3 = +ve$ (rise) ^{fall}
- $E_1 = +ve$ (rise)
- $I_4 R_4 = +ve$ (fall) ^{rise}

$$E_2 > E_1$$

• following figure shows a bridge network with the current as marked.

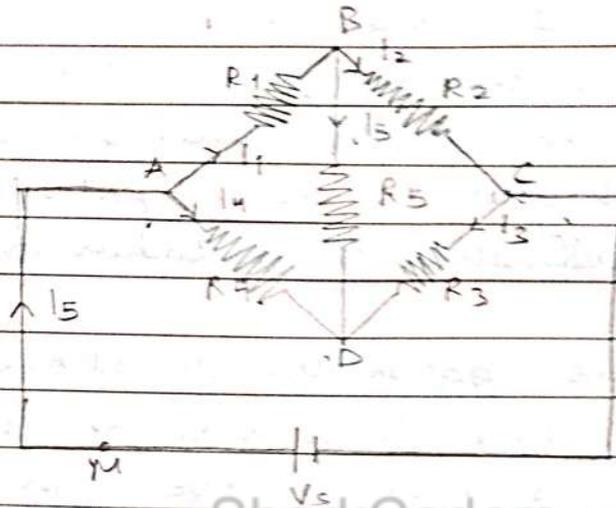- i) Write a KCL at 4 nodes
- ii) Write a KVL at meshes in ABDA, then BCDB
- iii) ~~BCDB~~ ADCMA



Ans. i) At node A,

$$I_5 = I_1 + I_4$$

At node B,

$$I_1 = I_2 + I_5$$

At node C,

$$I_2 = I_3 + I_5$$

At node D,

$$I_3 = -I_4 - I_5$$

$$I_3 + I_4 + I_5 = 0$$

For mesh ABDA,

$$-I_1 R_1 - I_5 R_5 + I_4 R_4 = 0$$

For mesh BCDB,

$$-I_2 R_2 - I_3 R_3 + I_5 R_5 = 0$$

For mesh ADCMA,

$$-I_4 R_4 + I_3 R_3 + V_s = 0$$

$$\begin{aligned}
 \textcircled{1} \quad E_1 - I_1 R_1 - R_2(I_1 - I_3) - R_2(I_1 - I_2) &= 0 \\
 E_1 - I_1 R_1 - I_1 R_2 + I_3 R_2 - I_1 R_2 + I_2 R_2 &= 0 \\
 E_1 - (R_1 + R_2 + R_3) I_1 + I_2 R_2 + I_3 R_3 &= 0 \\
 -(R_1 + R_2 + R_3) I_1 + I_2 R_2 + I_3 R_3 &= -E_1 \\
 (R_1 + R_2 + R_3) I_1 + I_2 R_2 + I_3 R_3 &= E_1
 \end{aligned}$$

Apply KVL for Mesh 2.

$$\begin{aligned}
 E_2 - R_2(I_2 - I_1) - R_5(I_2 - I_3) - R_4 I_2 &= 0 \\
 E_2 - I_2 R_2 + I_1 R_2 - I_2 R_5 + I_3 R_5 - I_2 R_4 &= 0 \\
 E_2 - I_1 R_2 - (R_2 + R_4 + R_5) I_2 + I_3 R_5 &= 0 \\
 R_2 I_1 - (R_2 + R_4 + R_5) I_2 + I_3 R_5 &= -E_2 \\
 -R_2 I_1 + (R_2 + R_4 + R_5) I_2 - I_3 R_5 &= E_2
 \end{aligned}$$

Apply KVL for Mesh 3.

$$\begin{aligned}
 E_3 - R_3(I_3 - I_1) - R_6 I_3 - R_7 I_3 - R_5(I_3 - I_2) &= 0 \\
 E_3 - I_3 R_3 + I_1 R_3 - I_3 R_6 - I_3 R_7 - I_3 R_5 + I_2 R_5 &= 0 - E_3 \\
 E_3 = I_3 R_3 - I_1 R_3 + I_3 R_6 + I_3 R_7 + I_3 R_5 - I_2 R_5 & \\
 E_3 = I_3 (R_3 + R_6 + R_7 + R_5) - I_1 R_3 - I_2 R_5 & :
 \end{aligned}$$

Arrange in matrix form,

$$\begin{bmatrix} (R_1 + R_2 + R_3) & -R_2 & -R_3 \\ -R_2 & (R_2 + R_4 + R_5) & -R_5 \\ -R_3 & -R_5 & (R_3 + R_5 + R_6 + R_7) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} E_1 \\ E_2 \\ E_3 \end{bmatrix}$$

$$[R] [I] = [V]$$

$$\begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} E_1 \\ E_2 \\ E_3 \end{bmatrix}$$

where R_{11} = self resistance of mesh 1
 R_{22} = self resistance of mesh 2
 R_{33} = self resistance of mesh 3

i.e. sum of all resistances in each mesh

R_{12} and R_{21} = sum of all resistances common to mesh 1 and mesh 2.

R_{23} and R_{32} = sum of all resistances common to mesh 2 and mesh 3.

SharkCoders

R_{31} and R_{13} = sum of all resistances common to mesh 1 and mesh 3


• if we assume each mesh current to flow in clockwise direction,

→ all self resistances will always be +ve.

→ all mutual resistances will always be -ve.

##

Q.

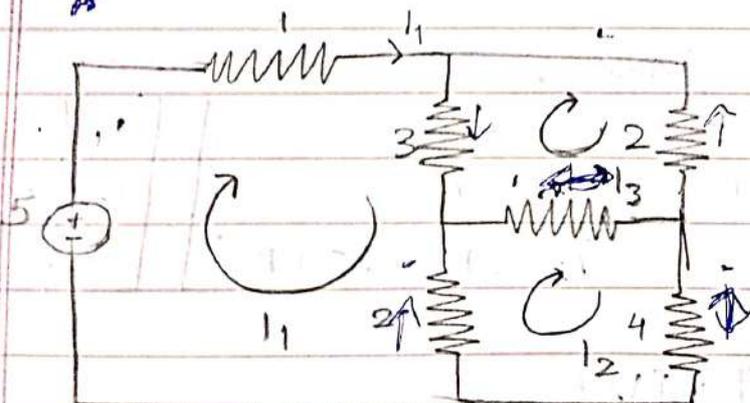

Apply to KVL to mesh 1,

$$5 - 1(i_1) - 3(i_1 - i_3) - 2(i_1 - i_2) = 0$$

$$5 - 4i_1 - 3i_1 + 3i_3 - 2i_1 + 2i_2 = 0$$

So ~~at~~

$$5 - 6i_1 + 2i_2 + 3i_3 = 0$$

$$6i_1 - 2i_2 - 3i_3 = 5$$

Apply to KVL to mesh 2,

$$E - i_3(2) - 3(i_3 - i_1) - 1(i_3 - i_2) = 0$$

$$E - 2i_3 = 3i_3 + 3i_1 - i_3 + i_2 = 0$$

$$E - 6i_3 + i_2 + 3i_1 = 0$$

$$6i_3 - i_2 - 3i_1 = E \quad -3i_1 - i_2 + 6i_3 = 5$$

Apply to KVL to mesh 3,

$$E + 2(i_2 - i_1) + 1(i_2 - i_3) + 4i_2 = 0$$


$$5 + 2i_2 - 2i_1 + i_2 + i_3 - 4i_2 = 0$$

$$5 - 2i_1 - i_2 + i_3 = 0$$

$$2i_1 + i_2 + i_3 = 5$$

6	-2	-3	i_1	=	5
3	1	-6	i_2	=	-5
2	1	1	i_3	=	5

$[R] \quad [i] = [V]$

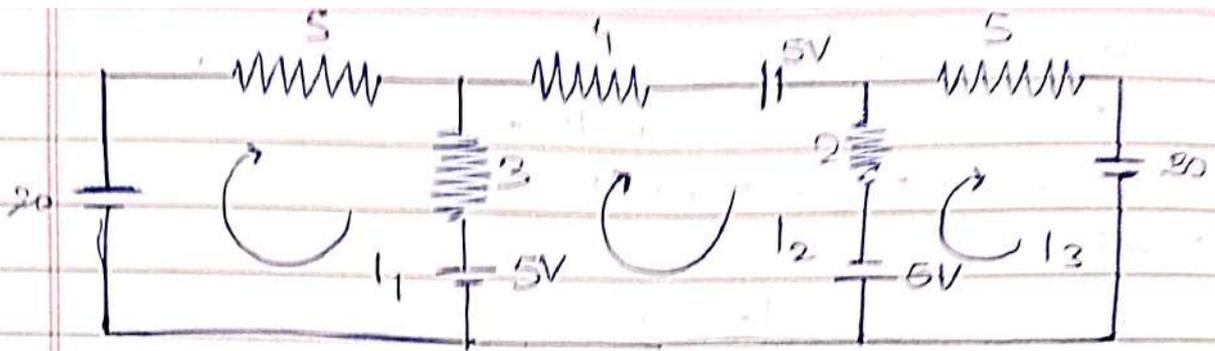

Each meshing in the circuit

Apply KVL to mesh 1.

$$20 - 5i_1 - 3(i_1 - i_2) - 5 = 0$$

$$20 - 5i_1 - 3i_1 + 3i_2 - 5 = 0$$

$$20 - 8i_1 + 3i_2 - 5 = 0$$

$$-8i_1 + 3i_2 + 15 = 0$$

$$8i_1 - 3i_2 = 15$$

Apply KVL to mesh 2,

$$5 - 3(i_2 - i_1) - 4i_2 + 5 - 2(i_2 - i_3) + 5 = 0$$

$$5 - 3i_2 + 3i_1 - 4i_2 + 5 - 2i_2 + 2i_3 + 5 = 0$$

$$15 - 9i_2 + 3i_1 + 2i_3 = 0$$

$$3i_1 + 2i_3$$

$$3i_1 - 9i_2 + 2i_3 = -15$$

$$-3i_1 + 9i_2 - 2i_3 = 15$$

Apply KVL to mesh 3,

$$-5 - 2(i_3 - i_2) - 8i_3 + 30 = 0$$

$$-5 - 2i_3 + 2i_2 - 8i_3 + 30 = 0$$

$$2i_2 - 10i_3 + 25 = 0$$

$$10i_3 - 2i_2 = 25$$

$$5i_3 - i_2 = 12.5$$

$$5 = 2i_2$$

$$10i_3 - 2i_2 = 25$$

higher to lower \rightarrow -ve (potential)

$$\begin{bmatrix} 8 & -3 & 0 \\ -3 & 9 & -2 \\ 0 & -2 & 10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 15 \\ 15 \\ 25 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 8 & -3 & 0 \\ -3 & 9 & -2 \\ 0 & -2 & 10 \end{bmatrix} = 0$$

$$= 8(90 - 4) + 3(-30 - 0) + 0$$

$$= 688 - 90$$

$$= 598$$

$$\Delta_1 = \begin{bmatrix} 15 & -3 & 0 \\ 15 & 9 & -2 \\ 25 & -2 & 10 \end{bmatrix} = 0$$

$$= 15(90 - 4) + 3(150 + 50) + 0$$

$$= 15 \times 86 + 3 \times 200$$

$$= 1290 + 600 = 1890$$

$$\Delta_2 = \begin{bmatrix} 8 & 15 & 0 \\ -3 & 15 & -2 \\ 0 & 25 & 10 \end{bmatrix}$$

$$= 8(150 + 50) - 15(-30 + 0) + 0$$

$$= 8 \times 200 + 450$$


$$= 1600 + 450 = 2050$$

$$\Delta_3 = \begin{bmatrix} 8 & -3 & 15 \\ -3 & 9 & 15 \\ 0 & -2 & 25 \end{bmatrix} = 2130 - 225 = 1905$$

$$= 8(225 + 30) + 3(-75 + 0) + 15(6 + 0)$$


$$= 8 \times 255 - 225 + 90 = 2040 - 225 + 90 = 1905$$

Cramer's Rule.

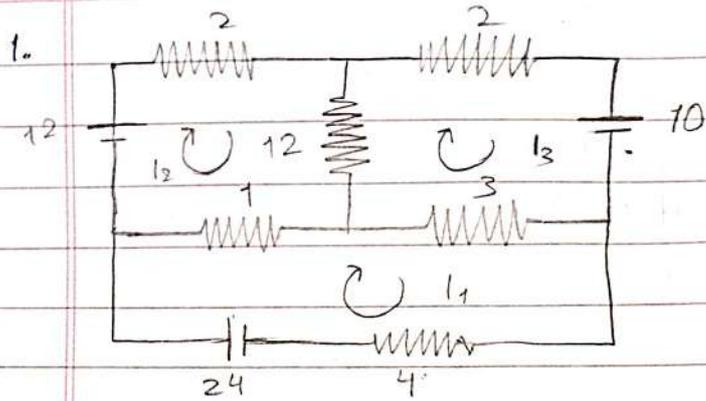

Determine current through 4Ω resistor.

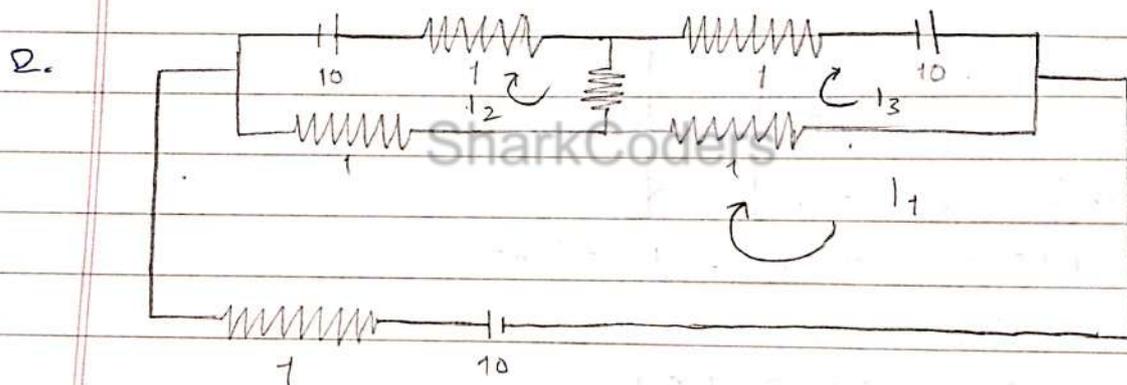
Ans. Apply KVL to mesh 1,
 $-4i_1 + 24 + 1(i_1 - i_2) + 3(i_1 - i_3) = 0$
 $-4i_1 + 24 + i_1 - i_2 + 3i_1 - 3i_3 = 0$
 $-3i_3 - i_2 + 24 = 0$
 $3i_2 + 3i_3 = 24.$



Find all the mesh currents.

Ans. Apply KVL to mesh 1,
 $10 - i_1$

Q3.

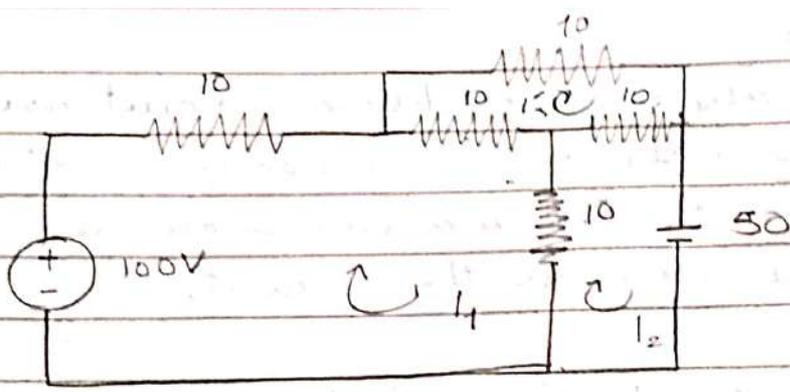

Find all the mesh currents

Ans.

Apply KVL to mesh 1,

$$100 - 10I_1 - 10(I_1 - I_3) - 10(I_1 - I_2) = 0$$

$$100 - 10I_1 - 10I_1 + 10I_3 - 10I_1 + 10I_2 = 0$$

$$100 - 30I_1 + 10I_2 + 10I_3 = 0$$

$$10 - 3I_1 + I_2 + I_3 = 0$$

$$3I_1 - I_2 - I_3 = 10$$

Apply KVL to mesh 2,

$$50 + 10(I_2 - I_1) - 10(I_2 - I_3) = 0$$

$$50 - 10I_2 + 10I_1 - 10I_2 + 10I_3 = 0$$

$$50 + 10I_1 - 20I_2 + 10I_3 = 0$$

$$-10I_1 + 20I_2 - 10I_3 = 50$$

Apply KVL to mesh 3,


$$-10(I_3 - I_2) - 10(I_3 - I_1) = 0$$

Nodal analysis

A method to analyze a complex circuit using KCL, to find the voltage in the electric circuit. As the name suggests, the analysis is carried out with reference to each node in the circuit.

- just the complement of mesh / loop analysis.
- in this analysis, the voltage drop is measured with respect to 2 nodes.
 - ^{first} is the main node.
 - second is the reference node.
- generally the grounded node is considered as the reference node.
- Steps to solve nodal analysis
 - select the reference node i.e. usually the ground ones
 - identify all the principle nodes in the circuit
 - all the nodes except the reference nodes are designated as V_1, V_2 , and so on.
 - assign the current to each branch. Express the branch current in terms of node voltages by using Ohm's Law.
 - apply KCL to all nodes (except reference) and write the nodal equation.
 - solve the KCL eqⁿ to get the node voltages.

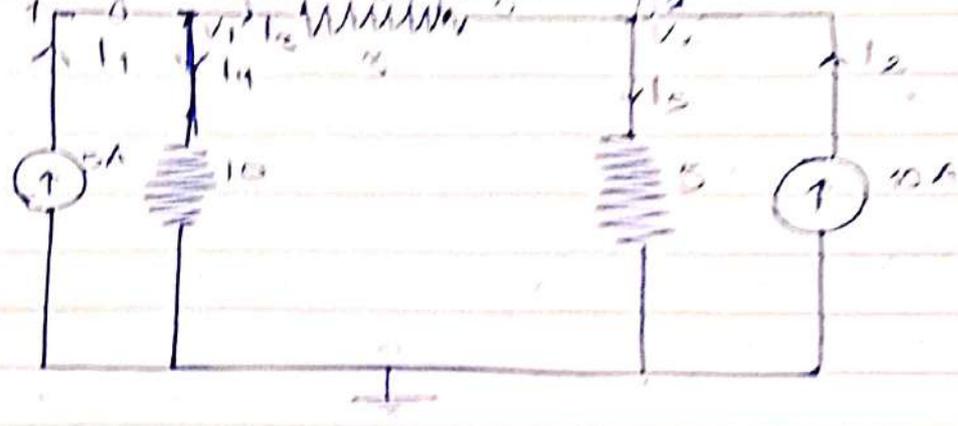Q) Determine the current in ammeter I_m using nodal analysis for the circuit shown.



Ans.

Ans. Apply KCL at node 1,

$$I_1 = (I_2) + (I_3)$$

$$5 = \left(\frac{V_1 - V_2}{5}\right) + \left(\frac{V_1}{10}\right)$$

$$5 = \frac{10V_1 - 10V_2 + 3V_1}{30}$$

$$5 = \frac{13V_1 - 10V_2}{30} \quad [\text{reference was the value of } 0]$$

$$150 = 13V_1 - 10V_2$$

$$13V_1 - 10V_2 = 150$$

$$13V_1 = 150 + 10V_2$$

Apply KCL at node 2,

$$I_2 = I_3$$

∴

$$I_2 = I_3$$

$$10 = \frac{V_2}{5} - \left(\frac{V_1 - V_2}{5}\right)$$

$$10 = \frac{2V_2 - V_1 + V_2}{5} \quad \frac{3V_2 - 5V_1 + 5V_2}{15} = 10$$

$$50 = 2V_2 - V_1$$

$$\frac{8V_2 - 5V_1}{15} = 10$$

$$8V_2 - 5V_1 = 150$$

$$-10V_2 + 13V_1 = 150$$

$$\hline -2V_2 + 8V_1 = 300$$

$$8V_1 - 2V_2 = 300$$

$$4V_1 - V_2 = 150$$

$$8V_1 - 2V_2 = 300$$

$$6V_1 = 300$$

$$V_1 = 50 = V_2$$

$$13V_1 - 10V_2 = 150$$

$$(-) \quad -5V_1 + 8V_2 = 150$$

$$\hline 18V_1 - 18V_2 = 0$$

$$18V_1 = 18V_2$$

$$V_1 = V_2$$

SharkCoders

$$13V_1 - 10V_2 = 150$$

$$(-) \quad -5V_1 + 8V_2 = 150$$

$$\hline 18V_1 - 18V_2 = 0$$


$$V_1 = V_2$$

Q. Find the I in each branch using nodal analysis

$$I_{10} = \frac{50}{10} = 5$$

$$I_5 = \frac{V_2}{5} = \frac{50}{5} = 10$$

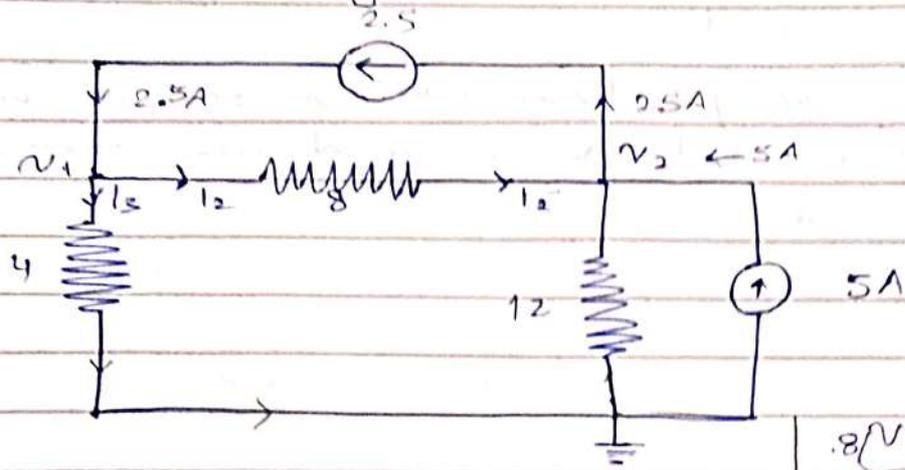Q. Determine the node voltage in the circuit using nodal analysis.



$$V_2 = I_1 + 2.5 - I_2$$

$$V_1 = I_2 + I_3 - 2.5$$

$$V_1 = I_2 + I_3 - 2.5$$

$$V_2 = -5 - I_2 + 2.5$$

$$V_1 = I_2 + I_3 - 2.5$$

$$V_2 = -I_2 - 2.5$$

$$V_1 = \frac{V_1}{8} + \frac{V_1}{4} - 2.5$$

$$V_1 = \frac{V_1 + 2V_1 - 10}{8}$$

$$8V_1 = 3V_1 - 10$$

$$5V_1 = -10$$

$$V_1 = -2$$

$$V_2 = -I_2 + 2.5$$

$$V_2 = \frac{V_1}{8} - 2.5$$

$$8V_2 = V_1 - 20$$

$$8V_2 = -2 - 2.5$$

$$V_2 = \frac{-4.5}{8}$$

$$V_2 = 0.25 - 2.5$$

$$V_2 = -2.25$$



$$V_1 = -2$$

1.


Q. Determine Res for the given circuit.

Source Transformation

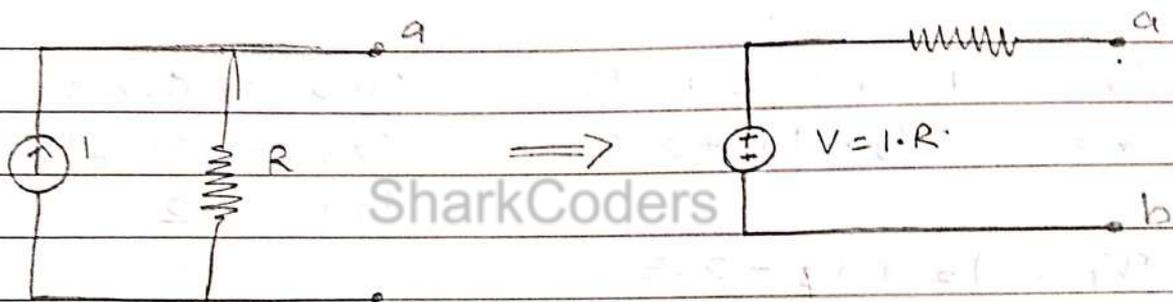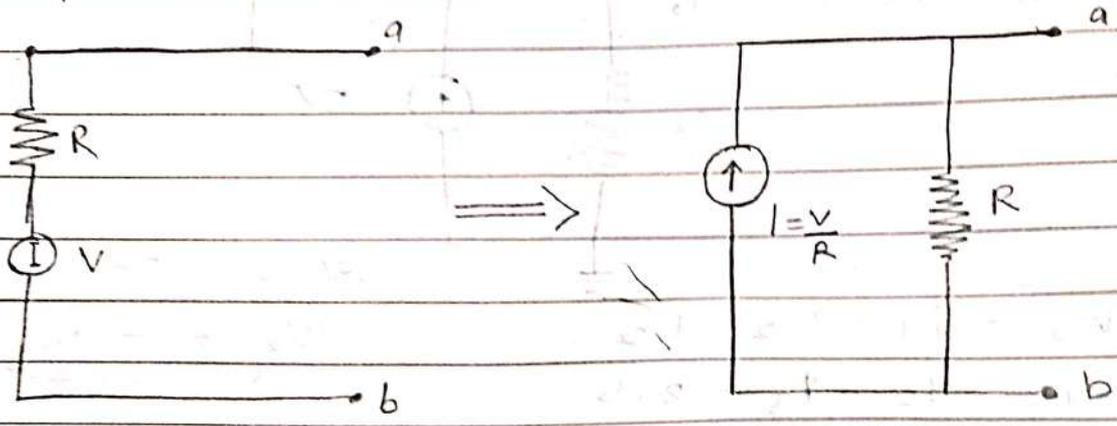
1. Conversion of practical voltage source into practical current source and vice versa.




2. Series connection of voltage source

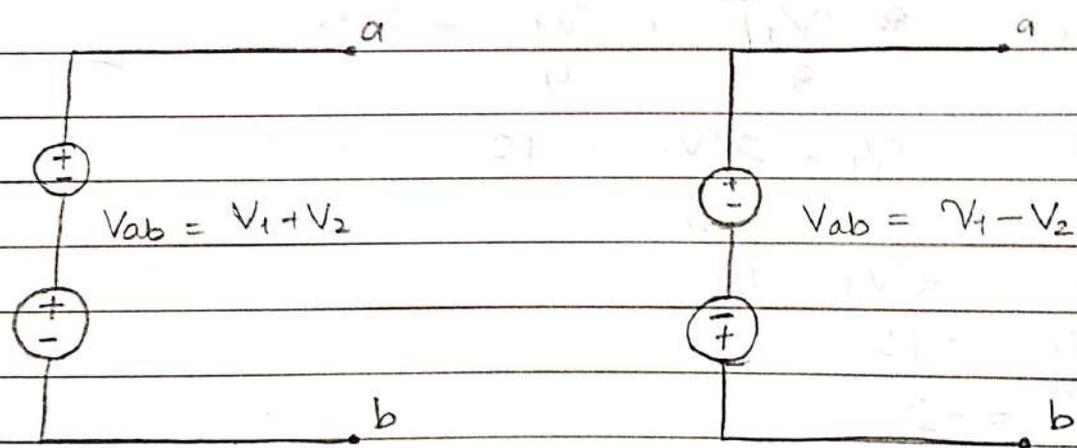


3. Parallel connection of current source

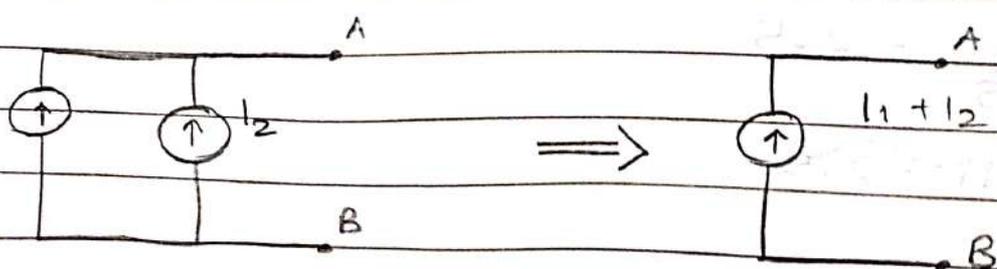


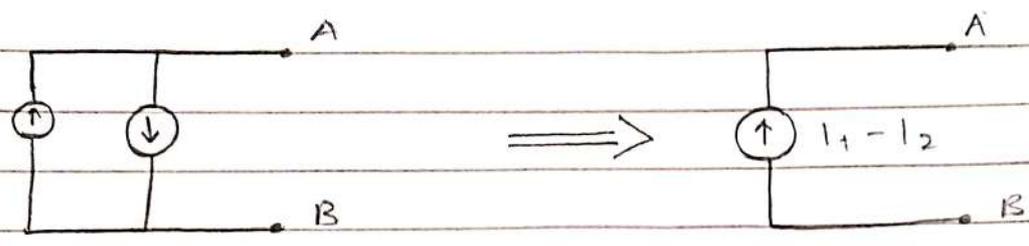

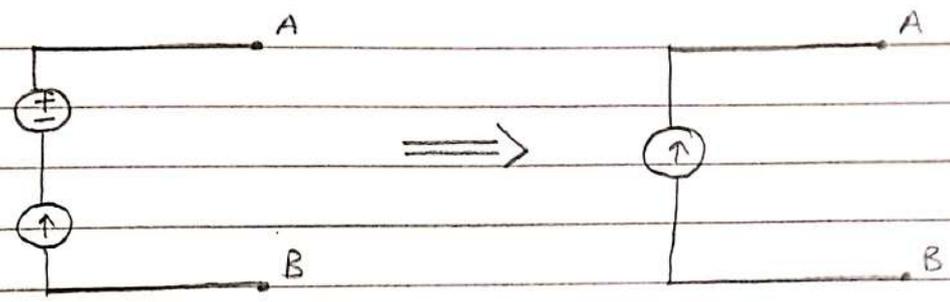4. Series combination of ideal voltage source and current source.




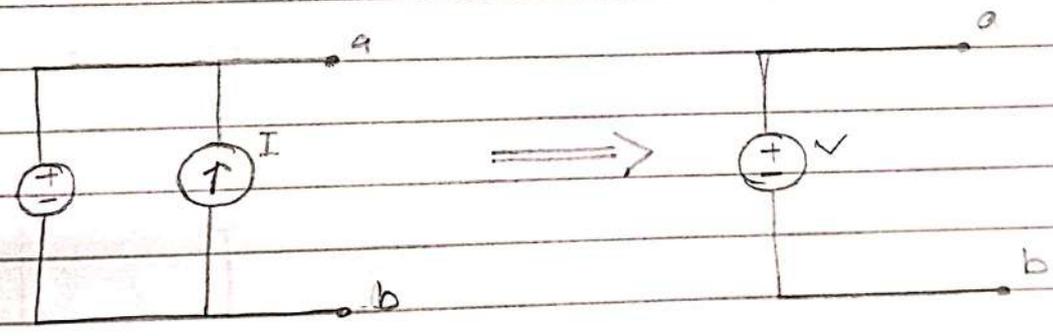5. Parallel combination of ideal voltage source and ideal current source



Q. Convert the combination into a single voltage source in series with a single element.

Ans.

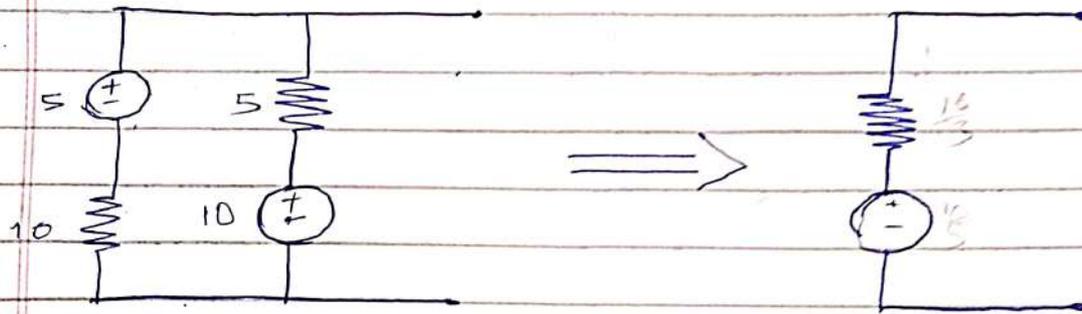


$$I' = \frac{V}{R} = \frac{5}{10} = 0.5$$

$$I = \frac{V}{R} = \frac{10}{5} = 2$$

$$I = \frac{V}{R} = \frac{10}{5} = 2$$

Q.

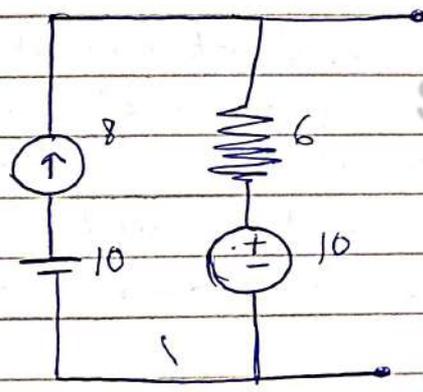


SharkCoders

Q. Using source transformation find the V across 10 Ω resistor in the circuit shown below.

Ans.

Superposition Theorem

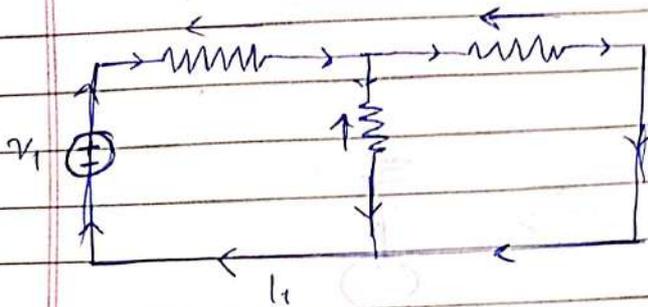


The superposition is applicable to all linear networks.


The procedure for analysing a circuit by superposition theorem is as follows:

- a) select any source in the circuit making the other source = 0.
- b) ~~the~~ Replace the V source by short circuit.
- a) Replace the current source by open circuit
- d) In obtaining the algebraic sum, if the current flows in the same direction, they add each other.
- e) However, if they are in opposite direction, they subtract from each other.

Q. Using the method of superposition, determine the current through a $5\ \Omega$ resistance for the circuit shown below.

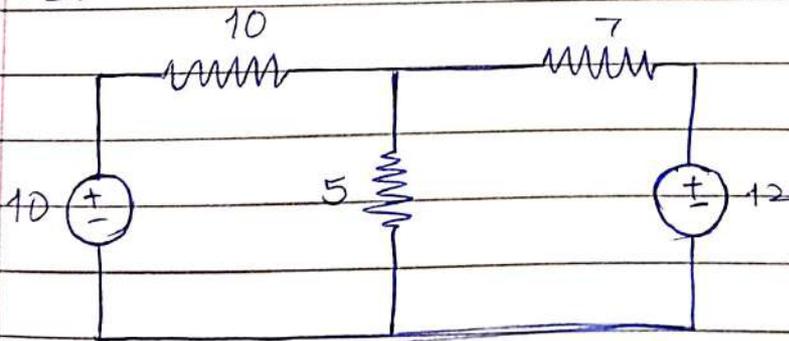

Case I: 10V Source acting alone.

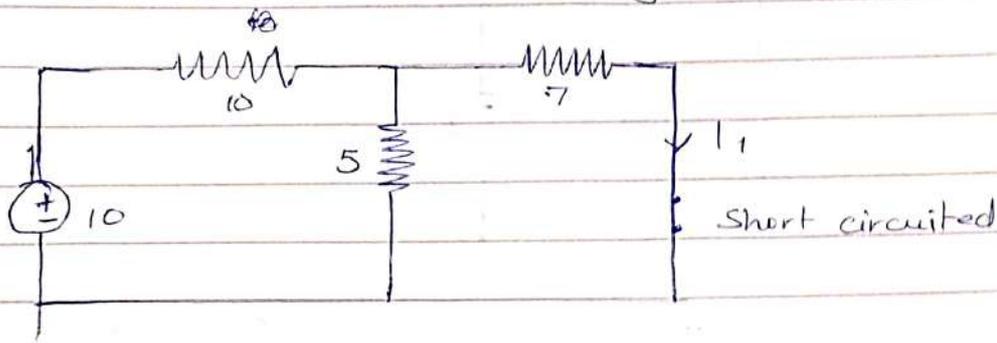

$$R_T = 10 + (5 || 7)$$


$$= 10 + \frac{5 \times 7}{5 + 7} = \frac{120}{12} + \frac{35}{12} = \frac{155}{12}$$

Total current

$$I_T = \frac{V}{R_T} = \frac{10}{12.92} = 0.77 \text{ A}$$

$$I_1 = I_T \times \frac{7}{5+7} = 0.77 \times \frac{7}{12} = \frac{5.39}{12} = 0.45 \text{ A}$$


Case II: 12V source acting alone.

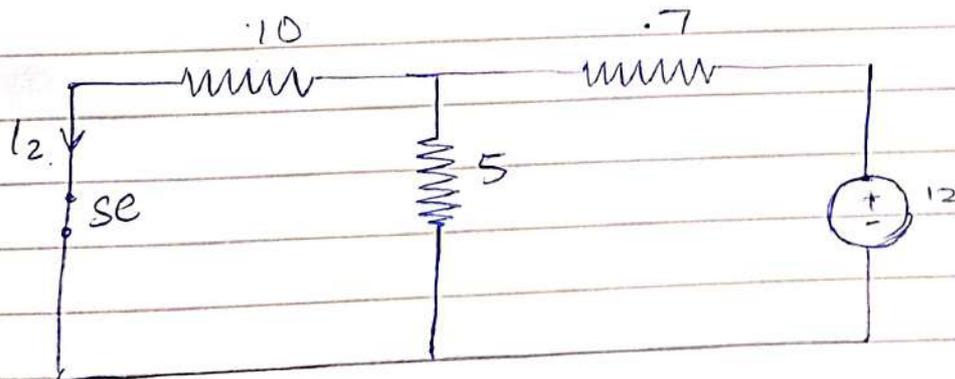

$$I_2 = I_T \times \frac{10}{10+5} = 0.77 \times \frac{10}{15}$$

Total current $I = I_1 + I_2 = 0.45 + 0.77 = 1.22$

$$I_T = 1.46$$

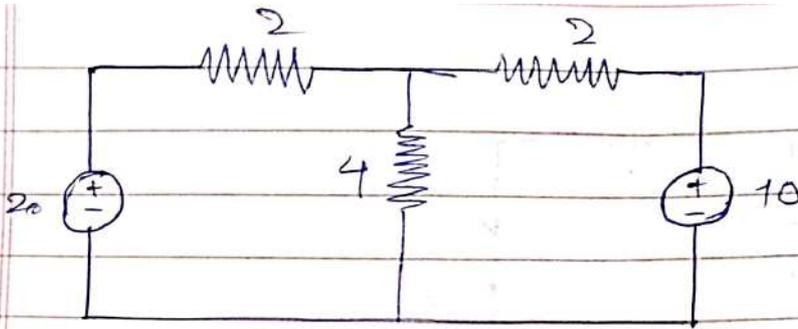

$$R_T = \cancel{20} 2 + \frac{4 \times 2}{6} = 2 + \frac{8}{6} = \frac{20}{6} = 3.34$$


$$I_T = \frac{V}{R_T} = \frac{20}{3.34} = 5.99$$

$$I_1 = I \times \frac{2}{6} = 2$$


$$R_T = 2 + \frac{8}{6} = 3.34$$

SharkCoders

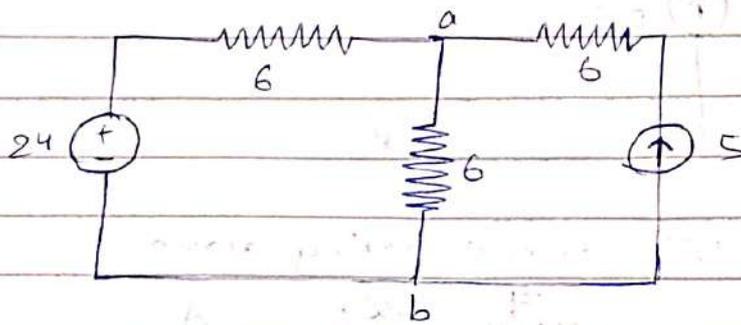Q. Determine the current I in the network by the principle of superposition.




Ans. Case I: 24V acting alone.

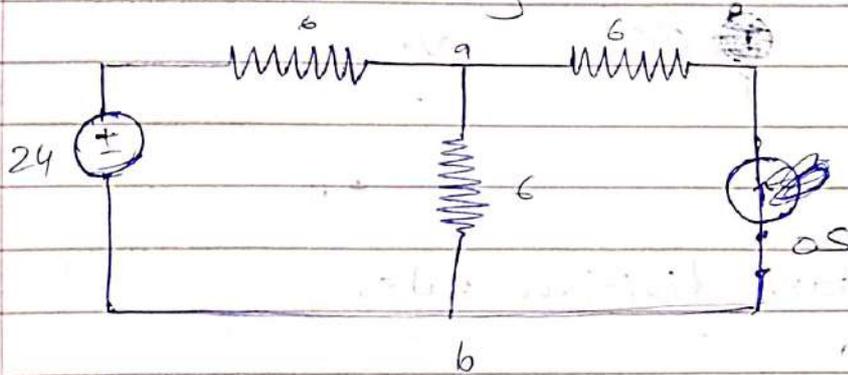


$$I_1 = \frac{V}{R} = \frac{24}{12} = 2$$

Case II: 5V acting alone

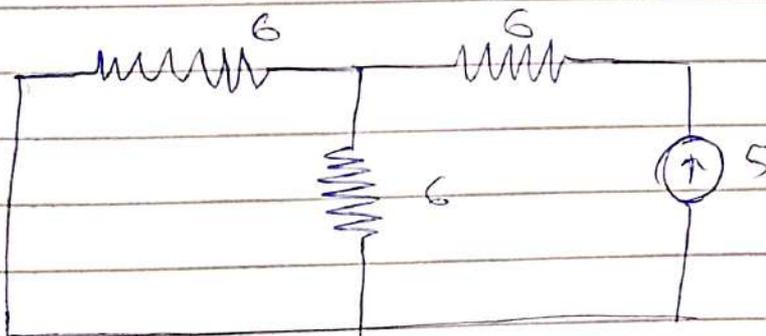


$$I_2 = \frac{5 \times 6}{6+6} = \frac{30}{12} = 2.5$$

$$I = I_1 + I_2 = 2 + 2.5 = 4.5$$

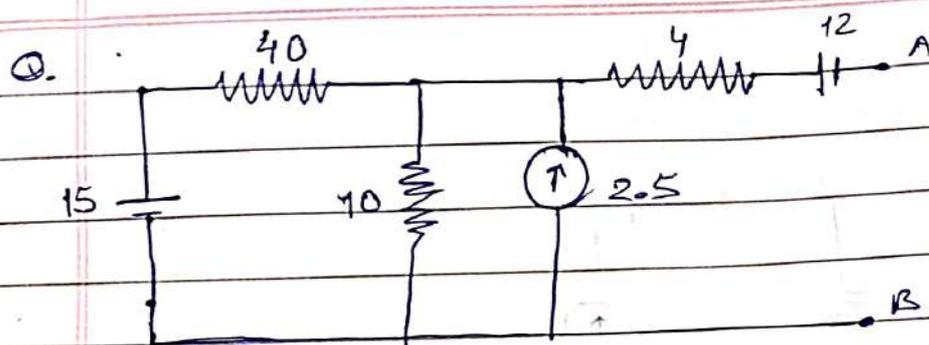

Case 1: When 15V source acting alone

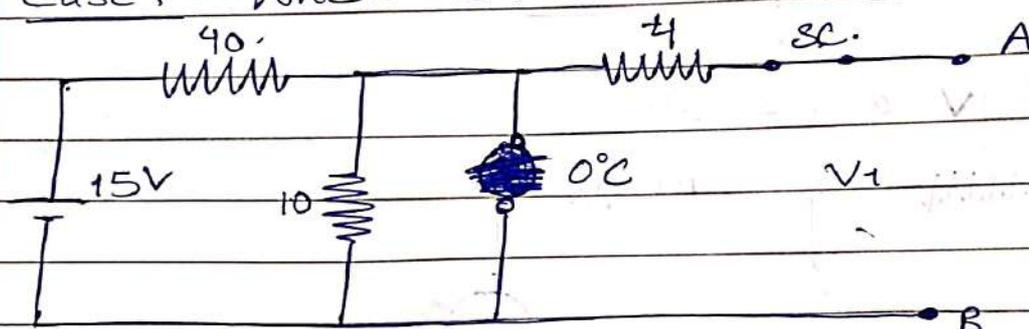


By using voltage division rule,


$$V_1 = 15 \times \frac{10}{10+40}$$

Q.

Q. Find the current in $23\ \Omega$ R in the circuit shown below.

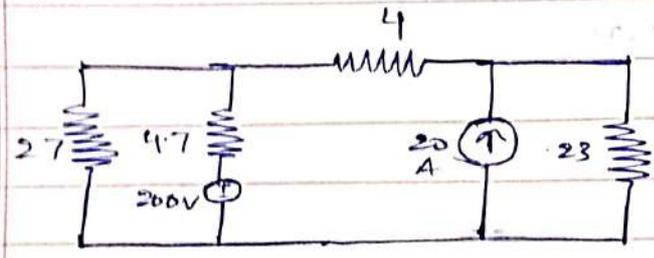

Case I: When 200V acts alone.

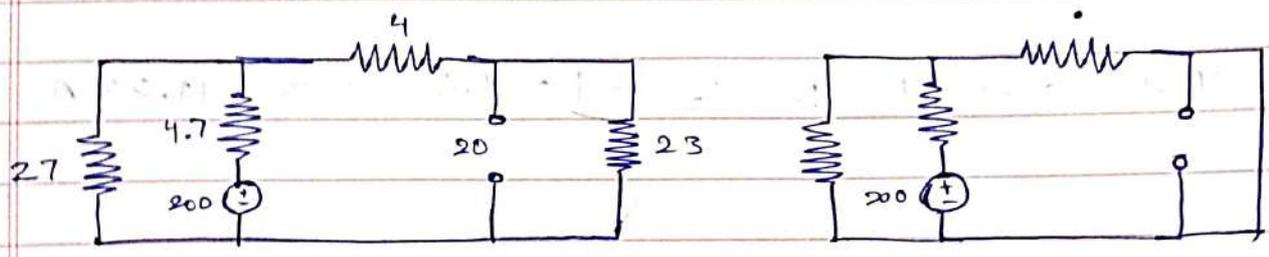

$$R_T = 4.7 + (27 \parallel 27)$$

$$= 4.7 + \frac{27 \times 27}{27 + 27} = 4.7 + 60.5$$


Total current

$$I_T = \frac{V}{R_T} = \frac{200}{60.5} = 3.31$$

By using CDR,

$$I_1 = I_T \times \frac{27}{54} = 1.65$$

Case II: 20A source acting alone

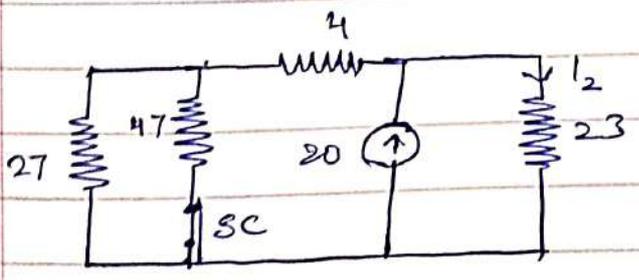

Total resistance

$$R_t = 4 + (27.47) \\ = 4 + \frac{27.47}{14} = 21.15$$

By using CDR,

$$I_2 = 20 \times \frac{21.15}{21.15 + 23} = 9.58$$

$$\text{Total current} = I_1 + I_2 = I = 1.65 + 9.58 = 11.23 \text{ A}$$

SharkCoders

Q. A ring shaped ~~core~~ electromagnet has an air gap of 6 mm and cross-sectional area of 12 cm^2 . The mean length of core is 60 cm. Calculate the mmf required to produce a flux density of 0.4 Wb/m^2 in the gap. Take $\mu_r = 400$.

Ans. Given

$$l_g = 6 \text{ mm} \\ = 6 \times 10^{-3} \text{ m}$$

$$a = 12 \text{ cm}^2 \\ = 12 \times 10^{-4} \text{ m}^2$$

$$l_i = 60 \text{ cm} \\ = 0.6 \text{ m}$$

$$B = 0.4 \text{ Wb/m}^2$$

$$\text{mmf} = ?$$

SharkCoders

$$\text{Flux } \phi = B \times a \\ = 0.4 \times 12 \times 10^{-4} \\ = 4.8 \times 10^{-4}$$

$$\therefore \phi = 4.8$$

$$\text{Total reluctance} = \frac{l_i}{\mu_0 \mu_r a} + \frac{l_g}{\mu_0 a} \\ = \left(\frac{l_i}{\mu_r a} + \frac{l_g}{a} \right) \frac{1}{\mu_0}$$

$$= \left(\frac{0.6}{400 \times 12 \times 10^{-4}} + \frac{6 \times 10^{-3}}{12 \times 10^{-4}} \right) \frac{1}{4\pi \times 10^{-7}}$$

$$= \left(\frac{60}{48} + 0.5 \times 10 \right) \frac{1}{4\pi \times 10^{-7}}$$

$$= 4976,114.65$$

Q. An iron ring of 50 cm mean length has an air gap of 1 mm and winding 200 turns. If the permeability of iron is 500, then current of 1 A flows through the coil, find the flux density.

Ans. Given

$$l_i = 50 \text{ cm} = 0.5 \text{ m}$$

$$l_g = 1 \text{ mm} = 1 \times 10^{-3} \text{ m}$$

$$N = 200$$

$$I = 1$$

$$B = ?$$

$$\phi = B \cdot a$$

$$\text{Total mmf} = H_i l_i + H_g l_g$$

$$H = \frac{B}{\mu_0 \mu_r}$$

$$= \frac{B l_i}{\mu_0 \mu_r} + \frac{B l_g}{\mu_0}$$

$$= \frac{B}{\mu_0} \left(\frac{l_i}{\mu_r} + l_g \right)$$

$$200 = \frac{B}{4 \times 3.14 \times 10^{-7}} \left(\frac{0.5}{500} + \frac{10^{-3}}{1} \right)$$

$$B = 7.96$$

Q. A ring composed of 3 sections of cross sectional area is 0.01 m^2 for each section. The mean arc lengths are 0.3 m, 0.2 m, 0.1 m. An air gap length of 0.1 mm cut in the ring. μ_r for ABC section are

Ans. Given

$$l_a = 0.3$$

$$\mu_{ra} = 5000$$

$$\phi = 7.5 \times 10^{-4} \text{ Wb / m}^2$$

$$l_b = 0.2$$


$$\mu_{rb} = 1000$$

$$l_c = 0$$

$$\mu_{rc} = 10000$$

Thevenin's Theorem

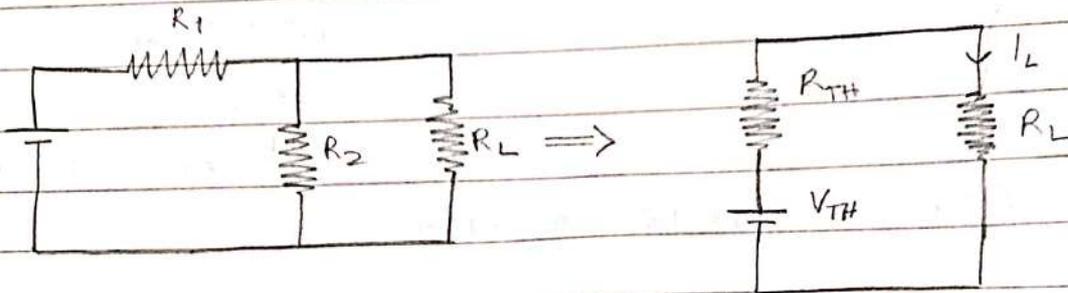It states that any two terminal network can be replaced by an equivalent circuit consisting of a voltage source (V_{TH}) in series with resistance (R_{TH}). The voltage V_{TH} is the open circuit voltage across these two terminals. R_{TH} is the resistance seen through the network across these two terminals.





Thevenin's equivalent circuit

$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

Steps to obtain Thevenin's equivalent circuit

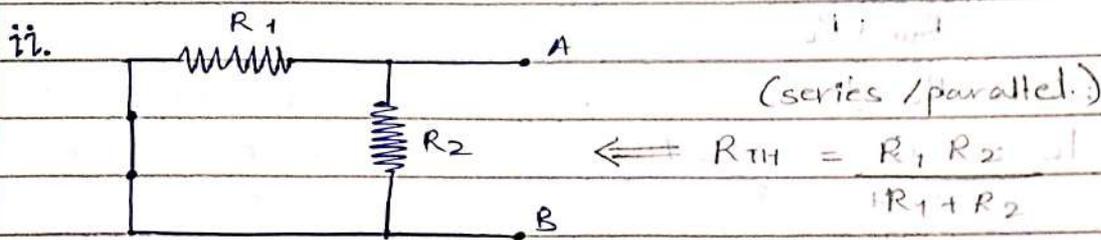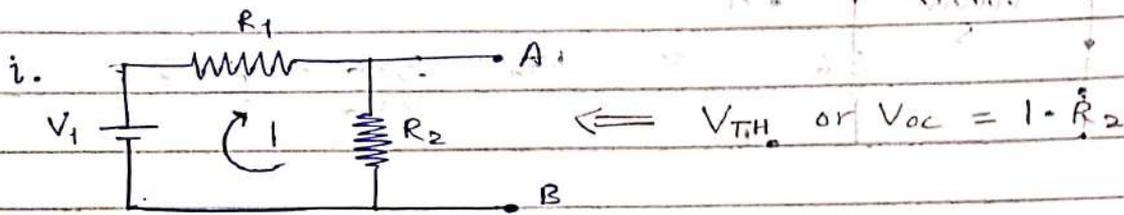1. Temporarily remove the load resistance (R_L) whose current is required.
2. Find the open circuit voltage (V_{OC}) which appears across the two terminals from where the load resistance has been removed. It is also called as thevenin's voltage (V_{TH}).
3. Calculate the resistance of whole network from the terminals after all the voltage source are replaced by short circuit and all the current sources replaced by open circuit. It is also called R_{TH} .
4. Replace the entire network by a single thevenin's voltage source whose voltage is V_{TH} and ~~whose~~ whose


resistance is R_{TH} as shown in figure. (i)




5. Connect the load resistance R_L back to its terminal from where it was previously removed.

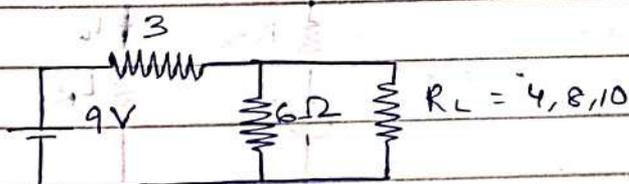6. Finally calculate the current flowing through load resistance by using eqⁿ $I_L = \frac{V_{TH}}{R_{TH} + R_L}$

Q. Consider a circuit shown in following figure and determine the thevenin's equivalent circuit for the load resistance R_L . Then determine I_L if $R_L = 4\Omega$, 8Ω , 10Ω
(i) (ii) (iii)




Ans.

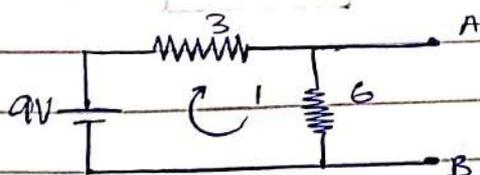 V_{TH} 1) Calculation of V_{oc} / V_{TH}

$$I = \frac{V}{R} = \frac{9}{3+L} = \frac{9}{9}$$

$$\therefore V_{TH} = 6V$$

2) Calculation for R_{TH}

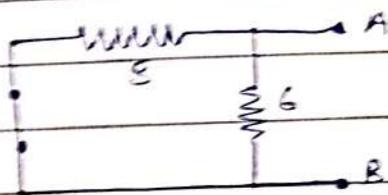

$$R_{TH} = \frac{3 \times 6}{3 + 6} = \frac{18}{3} = 2$$


$$\therefore I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

when $R_L = 4$

$$I_L = \frac{6}{2 + 4} = \frac{6}{6} = 1$$

$$\therefore I_2 = 1 \text{ A}$$


3) Thevenin's equivalent circuit

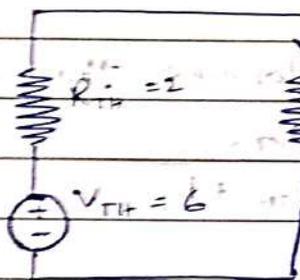


when $R_L = 8$

$$I_L = \frac{2 \times 8}{2 + 8} = 0.6$$

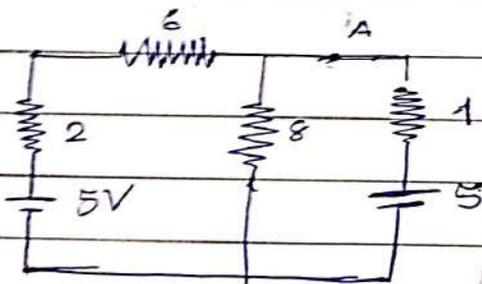
C. Determine the Thevenin's equivalent circuit between terminals A and B for the circuit shown below.



\Rightarrow

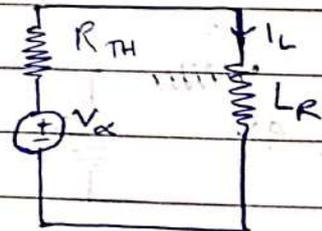

Ans.

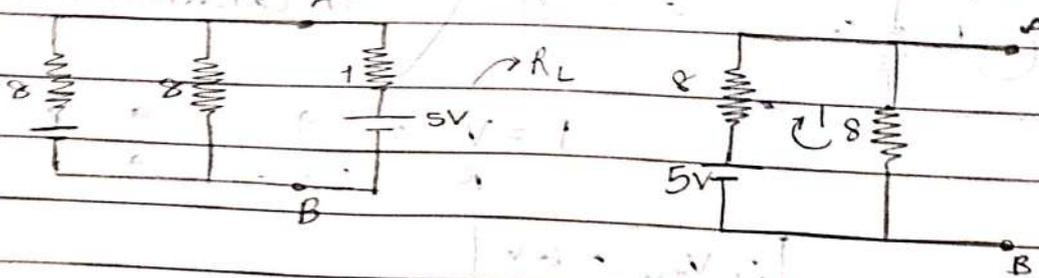

1) Calculation of V_{TH} (circuit diagram is given)

$$I = \frac{V}{R} = \frac{5}{4} = 1.25$$

(d) full circuit diagram

$$V_{TH} = 8 \times I = 8 \times 1.25 = 10$$

$$\therefore V_{TH} = 10$$

2) Calculations of R_{TH}

$$R_{TH} = \frac{8 \times 8}{8+8} = \frac{64}{16}$$

$$= 4$$


$$I_L = \frac{V_{TH}}{R_{TH} + R_L} = \frac{10}{4+1}$$

$$= 2$$

SharkCoders

Norton's Theorem.


It states that any two terminals of an active resistance network may be represented by a parallel combination of current source and resistors. The value of the current source is a short circuit current at the terminals and the value of the equivalent resistance seen looking back into the network with all energy sources replaced by their respective internal resistances.

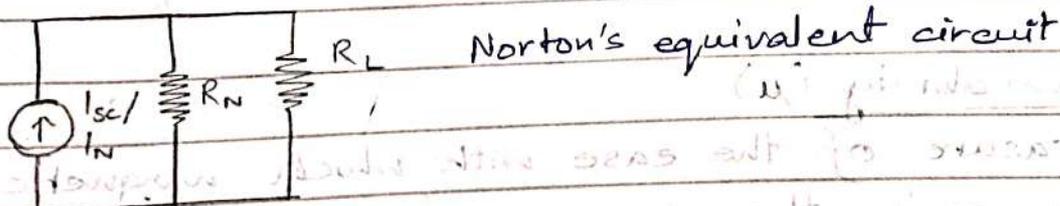

Unit III: Magnetic Circuits

Magnetic Flux (ϕ)

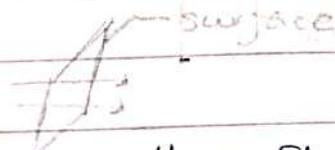Number of magnetic lines of force or the normal component of magnetic field passing through the surface of specified area.



- more the lines of force, greater the flux and stronger the magnetic field.

$$\phi \propto B$$

→ SI unit - Weber (Wb)

$$\phi = B \cdot A$$

$$\rightarrow \phi = \vec{B} \cdot \vec{A}$$

→ B = magnetic flux density

→ A = area of surface

$$\cdot \phi = BA \cos \theta$$

Magnetic flux density (B)

- Amount of magnetic flux per unit area of surface taken perpendicular to the direction of magnetic flux

→ SI unit - Wb m^{-2}

- B is a measure of the ^{density} strength of a magnetic field at a given point.

$$\rightarrow B = \frac{\phi}{A} \quad \left[T = \frac{\text{Wb}}{\text{m}^2} \right]$$

Permeability (μ)

Measure of the ease with which magnetic lines of force passing through a given material.

- magnetic permeability \propto conductivity of magnetic lines of force

• Definitions - Unit III & IV ✓

• Derivations - avg } Unit IV ✓

- rms } ✓

- Unit III ✓

- elect. circ. & mag. circ. ✓

①

SharkCoders

Energy stored in mag. field.

Series mag. field

Assignment

• Notes sent for Unit IV

• Capacitor and all circuits derivation

STAH.com

www.STAH.com

• e.g. soft iron has high permeability

• SI unit - Henry (meter) (H/m)

$$\mu = \frac{B}{H} \quad \left[\begin{array}{l} H = \text{magnetic field strength} \\ \mu = \text{permeability} \end{array} \right]$$

• μ of free space / vacuum = μ_0

$$\mu_0 = 4\pi \times 10^{-7} \left(\frac{H}{m} \right)$$

Relative μ

Measure of relative ease with which a given ^{material} conducts magnetic flux compared with the conduction of flux in air.

• $\mu = 1$ for air / vacuum

Absolute permeability

μ of a non-magnetic material such as air, copper, wood, glass, etc. is ^{usually} equal to unity.

μ of magnetic materials such as Co, Ni, Fe, steel, and alloys ^{is} greater than 1 and is not constant.

Magnetic field strength (H)

Ratio of the mmf (magneto-motive force) which is required to create a certain flux density within a certain material per unit length of that material.

• $\text{mmf} = NI$

• $\text{mmf} = NI$

• $H = \frac{NI}{l}$ $\left[H = \frac{A \cdot T}{m} \right]$ where $A = \text{ampere}$
 $I = \text{turns}$
 $l = \text{length}$

• H at any point within a magnetic field is numerically equal to the force experienced by a north pole of 1 Wb placed at that point.

• $B \propto H$

$\frac{B}{H} = \text{constant} = \mu$

$H = \frac{B}{\mu}$ [$\mu = \text{absolute permeability of medium}$]

Reluctance

• Property of a material which opposes the magnetic flux in it.

• analogous to resistance

• reluctance (S) = $\frac{\text{MMF}}{\text{flux}} = \frac{AT}{Wb}$

• $S = \frac{l}{\mu_0 \mu_r a}$

[$l = \text{length}$

$\mu_0 = \mu$ of vacuum.

$\mu_r = \text{relative } \mu$

$a = \text{area of cross-section}$]

• SI unit - $AT \cdot Wb^{-1}$

Permeance

Reciprocal of ~~reluctance~~ reluctance

• analogous to conductance

• property of a material which ~~carries~~ conducts the ϕ in it.

• permeance = $\frac{1}{\text{reluctance}} = \frac{\mu_0 \mu_r a}{l}$

• SI unit - $\text{Wb} \cdot \text{A}^{-1} \cdot \text{T}^{-1}$

Q. The area of the face of pole shoe is 1.5 cm^2 and the total flux is 0.18 mWb . Calculate the flux density in air gap.

Ans. $A = 1.5 \text{ cm}^2 = 1.5 \times 10^{-4} \text{ m}^2$

$\phi = 0.18 \text{ mWb} = 0.18 \times 10^{-3} \text{ Wb}$

$B = ?$

$B = \frac{\phi}{A} = \frac{0.18 \times 10^{-3}}{1.5 \times 10^{-4}} = 0.12 \times 10 = 1.2 \text{ Wb m}^{-2}$

Q. A coil of 100 turns is wound uniformly over an iron ring with a mean circumference of 2 m and a uniform sectional area of 0.025 cm^2 . If the coil carries a current of 2 A , calculate.

i. mmf of circuit

ii. ~~use~~ H (magnetic field strength)

iii. B (magnetic field density)

iv. ϕ (magnetic flux)

Aus. $N = 100$

$$a = 0.025 \text{ cm}^2 = 0.025 \times (10^{-2})^2 \text{ m}^2$$
$$= 0.025 \times 10^{-4} \text{ m}^2$$

$$I = 2 \text{ A}$$

$$\text{i. } \text{mmf} = NI$$
$$= 100 \times 2$$
$$= 200 \text{ AT}$$

\therefore The mmf is of 200 AT.

$$\text{ii. } H = \frac{B}{\mu_0} = \frac{\text{mmf}}{l} = \frac{NI}{l} = \frac{200}{2} = 100 \text{ AT/m}$$

$$\text{iii. } B \propto H$$

$$B = \mu_0 H$$

$$B = 4\pi \times 10^{-7} \times 100$$

$$= 4\pi \times 10^{-5}$$

$$= 12.56 \times 10^{-5} \text{ Wb/m}^2$$

\therefore The magnetic field density is $12.56 \times 10^{-5} \text{ Wb/m}^2$

$$\text{iv. } \phi = B \cdot A$$

$$= 12.56 \times 10^{-5} \times 0.025 \times 10^{-4}$$

$$\phi = 0.314 \times 10^{-9} \text{ Wb}$$


\therefore The magnetic flux is $0.314 \times 10^{-9} \text{ Wb}$

• How to take length?

• $\mu_0 = ?$ 1 OR 4π?

• Is length = circumference

Magnetic field of a straight conductor

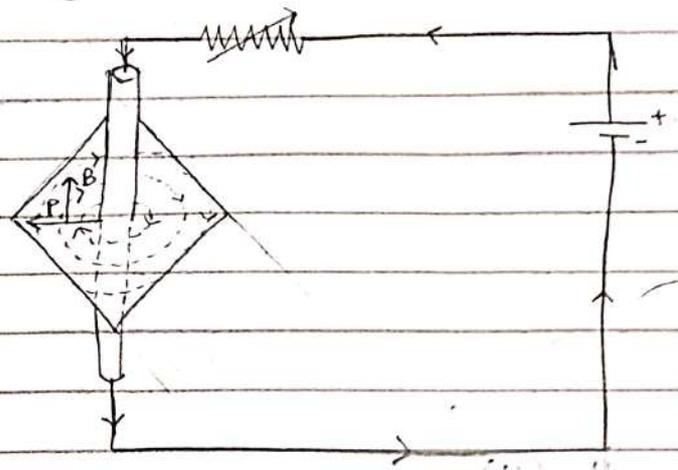

The magnetic field is in concentric circles around the straight conductor.

Let,

H = magnetic field strength at point P.

r = \perp distance of point P from the centre of the conductor.

I = current flowing through conductor

SharkCoders

Work done = $H \times \text{circumference}$

= $H \times 2\pi r$

= $2\pi r H$ joules

W.D = flux cut by the conductor.

Direction of current in conductor (dot & cross convention)




○ - conductor with no current

⊙ - conductor carrying current towards observer.

⊕ - conductor carrying current away from observer.

Magnetic Circuit

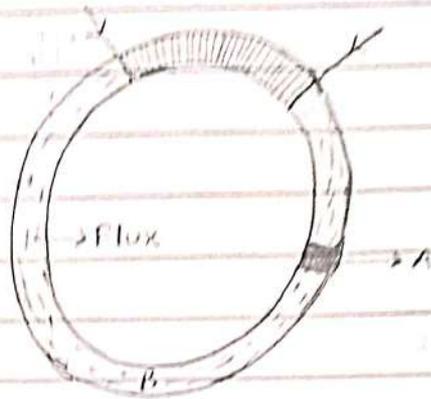

• Magnetic field strength (H)

$$H = \frac{\text{MMF}}{l} = \frac{NI}{l} \quad \text{AT m}^{-1}$$

• $\phi = \frac{\text{MMF}}{\text{reluctance}} = B \times A \cos \theta = \frac{NI}{S}$

SharkCoders

But $B = \mu_0 \mu_r (H)$

$$\Rightarrow B = \mu_0 \mu_r \left(\frac{NI}{l} \right) \quad \text{Wb m}^{-2} \quad \text{--- (1)}$$

Total ϕ produced.

$$\phi = B \times A = \left(\frac{\mu_0 \mu_r NI}{l} \right) (A) \quad \text{Wb} \quad \text{--- [From (1)]}$$

$$\therefore \phi = \frac{NI}{\frac{l}{\mu_0 \mu_r A}} \quad \text{--- (2) where } NI = \text{MMF} \quad \frac{l}{\mu_0 \mu_r A} = \text{reluctance (S) of core}$$

Similarities between magnetic circuits and electric circuits

Electric

a) closed path followed by current

b) current is flown through a conductor

$$I = \frac{V}{R}$$

c) driving force for current is called emf (V).

d) $R \propto$ length of conductor

$$R = \frac{\rho l}{a}$$

e) current density is the rate of electric current flowing per unit area.

$$S = \frac{I}{a} \text{ A m}^{-2}$$

f) the KCL and KVL are applicable to the electric circuit

Magnetic

closed path followed by magnetic flux.

flux is line of force through the medium from N to S pole.

$$\phi = \frac{mmf}{S}$$

driving force for flux is mmf (AT)

$S \propto$ length of magnetic path

$$S = \frac{l}{\mu_0 \mu_r a}$$

flux density is the amount of magnetic flux per unit area.


$$B = \frac{\phi}{A}$$

the Kirchoff's flux and mmf laws are applicable to the magnetic circuit.

Differences between magnetic circuit and electric circuit

ELECTRIC	MAGNETIC
a) electric current flows in an electric circuit.	Φ does not flow but it is setup in the magnetic circuit.
b) value of resistivity varies very slightly with temp. hence resistance of an electric current is practically constant.	value of μ_r is not constant for a given material, hence the 'S' of the magnetic circuit is not constant. Rather, it depends on flux density (B_i)
c) energy needed as long as current flows through electric circuit	once a magnetic flux is set up in circuit. No energy needed.
d) electric field lines do not form a loop.	magnetic field lines form a loop.

Simple Series magnetic field (circuit)

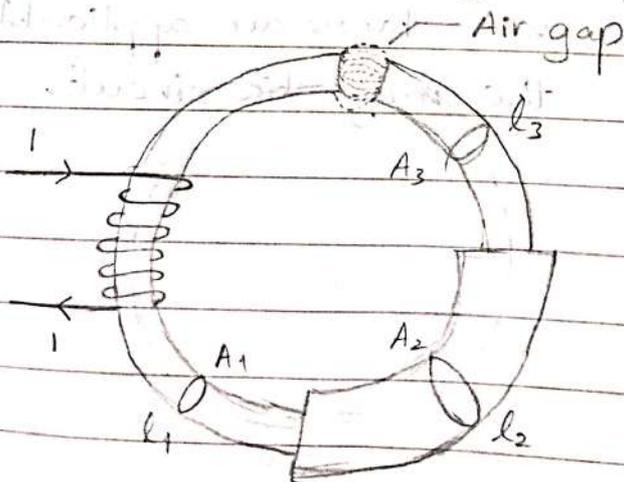

• Total reluctance = S_T

$$S_T = \frac{l_1}{\mu_0 \mu_{r1} A_1} + \frac{l_2}{\mu_0 \mu_{r2} A_2} + \frac{l_3}{\mu_0 \mu_{r3} A_3} + \frac{l_4}{\mu_0 A_4}$$

• Total mmf = $\text{mmf}_T = (\text{flux}) \times (\text{reluctance})$

$$\text{mmf}_T = \Phi \left(\frac{l_1}{\mu_0 \mu_{r1} A_1} + \frac{l_2}{\mu_0 \mu_{r2} A_2} + \frac{l_3}{\mu_0 \mu_{r3} A_3} + \frac{l_4}{\mu_0 A_4} \right)$$

$$\because \Phi = BA$$

$$\Rightarrow B = \frac{\Phi}{A}$$

$$\text{mmf}_T = \frac{B_1 l_1}{\mu_0 \mu_{r1}} + \frac{B_2 l_2}{\mu_0 \mu_{r2}} + \frac{B_3 l_3}{\mu_0 \mu_{r3}} + \frac{B l_4}{\mu_0}$$

$$\because H = \frac{B}{\mu_0 \mu_r}$$

SharkCoders


$$\ast \text{mmf}_T = H_1 l_1 + H_2 l_2 + H_3 l_3 + H_4 l_4$$

• In series magnetic circuit, magnetic flux (Φ) is the same in all the sections and all the equivalent reluctance of such magnetic circuit equals summation of the reluctance of an individual section.

• Consider a composite magnetic circuit of different magnetic material of different relative permeability along with an air gap as shown in fig.

• Therefore, the total ampere turns required for the entire series circuit is the sum of ampere turns of various parts.

Parallel magnetic circuit

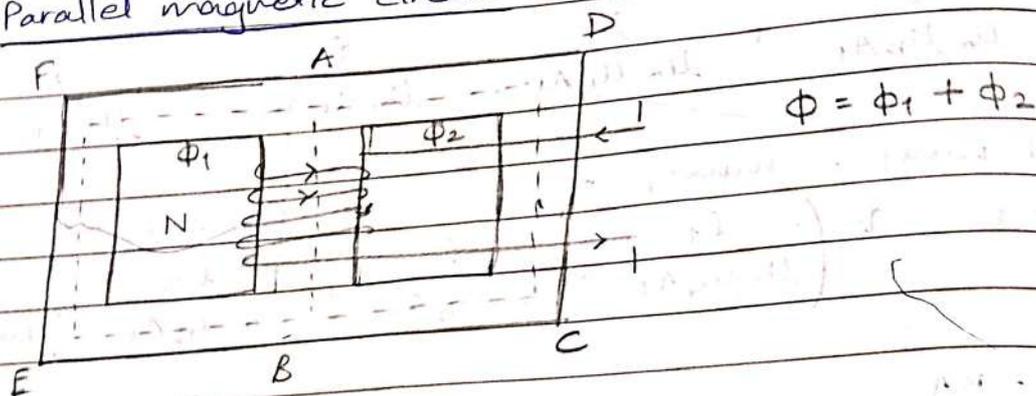

Total mmf required = mmf.

Total mmf required = (mmf required for path AB) + (mmf required for path ADCB)

OR

(mmf required for path ADCB)

Let S_c = reluctance of path AB

S_1 = reluctance of path AFEB

S_2 = reluctance of path ADCB

$$\therefore NI = \Phi_{sc} + (\Phi_1 S_1 \text{ or } \Phi_2 S_2)$$

$$\therefore \text{Total mmf} = \Phi_{sc} + \Phi_1 S_1 = \Phi_{sc} + \Phi_1 S_2$$

- a magnetic circuit has more than one path for magnetic flux.
- a coil of reluctance of N turns wound on central leg which carries a current of 1 ampere. The flux divides at A into two paths.
 - flux Φ_1 , along the path AFEB.
 - flux Φ_2 , along the path ADCB.

Q. A coil of insulated wire of 500 turns and of resistance $4\ \Omega$ is closely wound on an iron ring. The ring has mean diameter of $0.25\ \text{m}$ and uniform cross-sectional area of $700\ \text{mm}^2$. Calculate the total flux in the ring when a DC supply at $6\ \text{V}$ applied to the end of windings. Assume the $\mu_r = 550$.

Ans. Given

$$N = 500$$

$$R = 4\ \Omega$$

$$D = 0.25$$

$$l = \pi \cdot D = 3.14 \times 0.25 = 0.785\ \text{m}$$

$$a = 700\ \text{mm}^2 \times 10^{-6}\ \text{m}^2 = 7 \times 10^{-4}\ \text{m}^2$$

$$V = 6\ \text{V}$$

$$\mu_r = 550$$

$$\phi = ?$$

SharkCoders

Solⁿ

We know that,

$$\phi = B \times A$$

$$I = \frac{V}{R} = \frac{6}{4} = 1.5$$

Formula

$$H = \frac{NI}{l} = \frac{500 \times 1.5}{\pi \times 0.25} = 955.41\ \text{A m}^{-1}$$

$$\begin{aligned} B = \mu H &= \mu_0 \mu_r \cdot H \\ &= 4\pi \times 10^{-7} \times 550 \times 955 \\ &= 4\pi \times 55 \times 955 \times 10^{-6} \\ &= 659714 \times 10^{-6} \\ &= 0.659714 \\ &\approx 0.66 \end{aligned}$$

$$\phi = B \times A$$

$$= 0.66 \times 7 \times 10^{-4}$$

$$= 4.62 \times 10^{-4} \text{ Wb}$$

$$= 0.462 \times 10^{-3} \text{ Wb}$$

$$= 0.462 \text{ mWb}$$

Q. A ring shaped electromagnet has an air gap of 6 mm and cross-sectional area of 12 cm^2 . The mean length of the core is 60 cm. Calculate the mmf required to produce flux density of 0.4 Wb m^{-2} in the gap. Take $\mu_r =$

Ans. Given

$$l_g = 6 \text{ mm} = 6 \times 10^{-3} \text{ m}$$

$$a = 12 \text{ cm} = 12 \times 10^{-4} \text{ m}^2$$

$$l_i = 60 \text{ cm} = 0.6 \text{ m}$$

$$B = 0.4 \text{ Wb m}^{-2}$$

$$\text{mmf} = ?$$

SharkCoders

$$\text{Flux} \Rightarrow \phi = B \times A$$

$$= 0.4 \times 12 \times 10^{-4}$$

$$\phi = 4.8 \times 10^{-4} \text{ Wb}$$

$$\text{Total reluctance} = \frac{l_i}{\mu_0 \mu_r a} + \frac{l_g}{\mu_0 a}$$

$$= \frac{1}{\mu_0 a} \left(\frac{l_i}{\mu_r} + l_g \right)$$

$$= \frac{1}{4\pi \times 10^{-7} \times 12 \times 10^{-4}} \left(\frac{0.6}{400} + 6 \times 10^{-3} \right)$$

$$= \frac{1}{4.8 \times 10^{-11}}$$

$$= \left(1.5 \times 10^{-3} + 6 \times 10^{-3} \right) \times 10^{11} = 150.79 \times 10^{-8}$$

$$= \left(\frac{4.5 \times 10^{-2}}{150.79 \times 10^{-11}} + \frac{6 \times 10^{-3}}{150.79 \times 10^{-11}} \right)$$

$$= 9.94 \times 10^{-3} \times 10^8 + 0.039 \times 10^8$$

$$= 9.94 \times 10^5 + 39 \times 10^5$$

$$= 48.94 \times 10^5$$

$$S = 489.4 \times 10^4 \text{ AT Wb}^{-1}$$

$$\text{mmf} = S \times \phi$$

$$= 489.4 \times 10^4 \times 48 \times 10^{-4}$$

$$\text{mmf} = 2388.48 \text{ AT}$$

Q. An iron ring of 50cm mean length has an air gap of 1mm and winding of 200 turns. If permeability of iron is 500 then current of 1A close the coil, find the flux density. Assume $\mu_r = 500$

Ans. Given -
 $l_i = 50 \text{ cm} = 0.5 \text{ m}$
 $l_g = 1 \text{ mm} = 10^{-3} \text{ m}$
 $N = 200$
 $I = 1 \text{ A}$
 $B = ?$

Solⁿ
 Total mmf = $H_i l_i + H_g l_g$

$$\therefore H = \frac{B}{\mu_0 \mu_r}$$

$$\text{Total mmf} = \frac{B l_i}{\mu_0 \mu_r} + \frac{B l_g}{\mu_0 \mu_r}$$

$$\text{Total mmf (NI)} = B \left[\frac{l_i}{\mu_r \mu_0} + \frac{l_g}{\mu_0} \right]$$

$$200 \times 1 = B \left[\frac{0.5}{4\pi \times 10^{-7} \times 500} + \frac{10^{-3}}{4\pi \times 10^{-7}} \right]$$

$$200 = B \left[\frac{5 \times 10^{-1}}{4\pi \times 10^{-7} \times 500} + \frac{10^{-3}}{4\pi \times 10^{-7}} \right]$$

$$B = 0.1256 \text{ Wb m}^{-2}$$

Q. A ring composed of 3 sections. The cross section area is $a = 0.001 \text{ m}^2$ for each section the mean arc lengths are $l_a = 0.3 \text{ m}$, $l_b = 0.2 \text{ m}$, $l_c = 0.1 \text{ m}$ and air gap length $l_g = 0.1 \text{ mm}$ cut in the ring. μ_r for section a, b, c are $\mu_{ra} = 5000$, $\mu_{rb} = 1000$ and $\mu_{rc} = 10000$.

Flux in the air gap is $\phi = 7.5 \times 10^{-4} \text{ Wb}$. Find

i) mmf

ii) exciting current if coil has 100 turns

Ans. Given

$$a = 0.001 \text{ m}^2$$

$$l_a = 0.3 \text{ m}$$

$$l_b = 0.2 \text{ m}$$

$$l_c = 0.1 \text{ m}$$

$$\mu_{ra} = 500$$

$$\mu_{rb} = 1000$$

$$\mu_{rc} = 10000$$

$$\phi = 7.5 \times 10^{-4} \text{ Wb}$$